



# Verilog HDL – I

## Combinational Logic Circuit

黃元豪

Yuan-Hao Huang

國立清華大學電機工程學系

Department of Electrical Engineering

National Tsing-Hua University

# Outline

---



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits



# Introduction

- Verilog HDL是一種高階且模組化的硬體描述語言
  - 完整功能：整合電路描述、合成與模擬驗證之設計功能。
  - 彈性設計：模組化設計，易做重新組合，容易設計。
  - 多種描述型式：電路連接關係，順序性與共時性敘述，布林代數式等。
  - 跨平台可攜性：可用不同編譯軟體編譯，適用不同工作平台與製程。
  - 容易學習：語法與C語言相似。
- VHDL為另一個類似的硬體描述語言。



# Verilog HDL

- Verilog 硬體描述語言 (Verilog Hardware Description Language)
  - 在積體電路設計（特別是超大型積體電路的計算機輔助設計）的電子設計自動化領域中，**Verilog HDL**是一種用於描述、設計電子系統（特別是數位電路的硬體描述語言）。
  - Verilog HDL是電力電子工程師學會（IEEE）1364號標準。
- Verilog 硬體描述語言在邏輯設計上的用途
  - 用途一: 邏輯電路設計的模擬與驗證
  - 用途二: FPGA邏輯電路(\*\*IC電路)的設計與實作
    - \*\* IC電路的設計與實作在【EE4292積體電路設計實驗】教授。


# Verilog HDL Utilization Scenario I

- Simulation and verification of logic circuits on PC.

## Specification

2-to-1 Multiplexer

## Logic Design

 

## Verilog HDL Coding

```
module SMUX(out, a, b, sel);  
    output out;  
    input a,b,sel;  
    wire sel_n,t1,t2;  
  
    not U0(sel_n,sel);  
    and U1(t1,a,sel);  
    and U2(t2,b,sel_n);  
    or U3(out,t1,t2);  
  
endmodule
```

## Test Pattern

a, b, sel
000
001
010
...
111

Yes, it is correct !



Verilog HDL Simulator

- Imaging what happens when the circuit is as complex as a CPU or MP3 player processor.



# Verilog HDL Utilization Scenario II

- Design and Implementation of logic circuits in FPGA (IC)



Specification

2-to-1 Multiplexer

Verilog HDL Coding

```
module SMUX(out, a, b, sel);  
    output out;  
    input a,b,sel;  
    wire sel_n,t1,t2;  
  
    assign out = sel ? a:b;  
endmodule
```

Synthesized Logic Circuits

  

FPGA Implement Design and Programming



Now, it can work !

Verilog HDL Logic Synthesizer

# Outline

---




- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits

# Verilog Module Architecture



Device under Test (DUT)

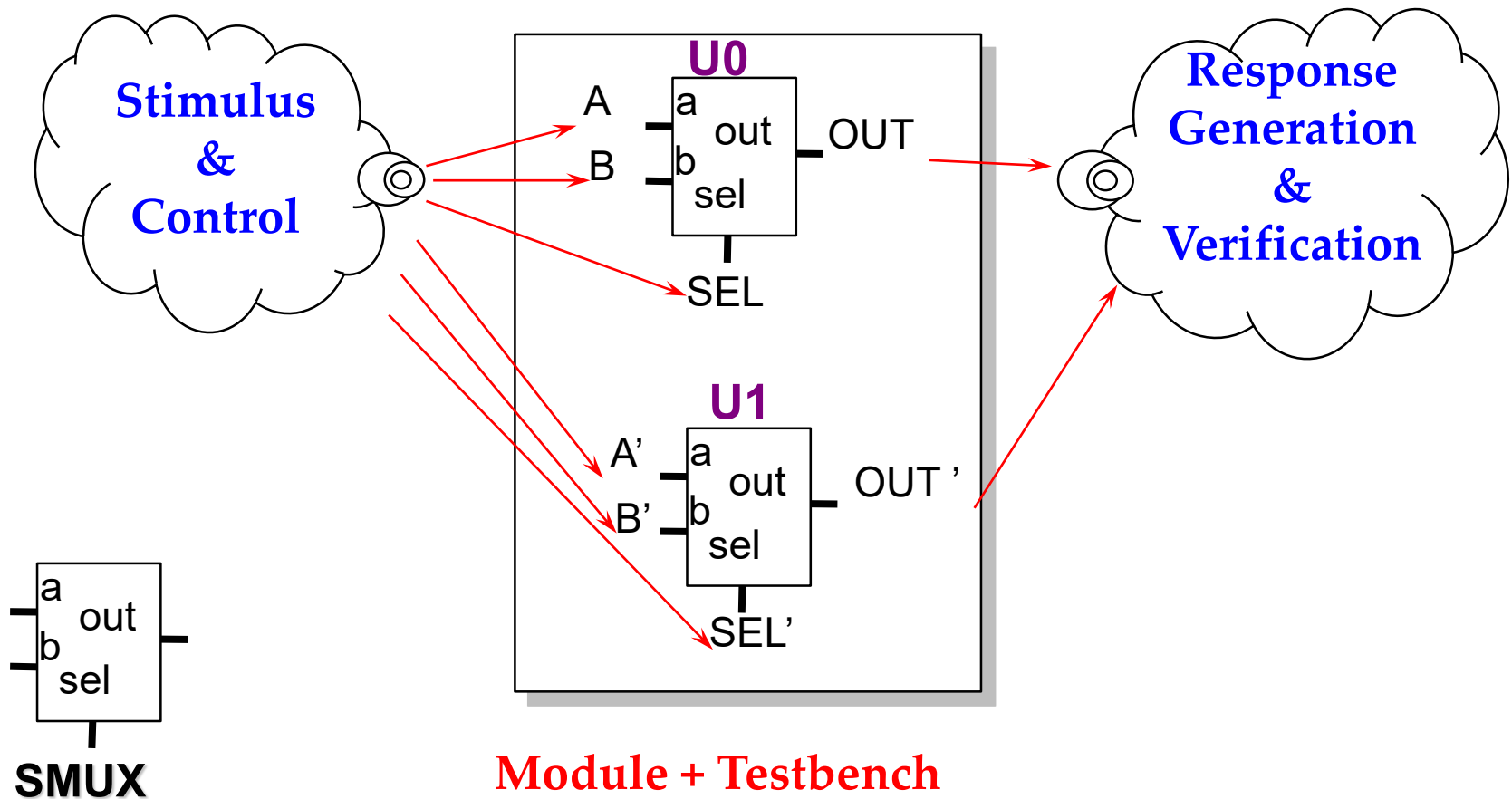





# Verilog Module

- `module module_name(port_names);`

- Port declaration

- Data type declaration

- Task & function declaration

- Module functionality or structure

- Timing Specification

- `endmodule`

```
module SMUX(out, a, b, sel);
```

```
output out;  
input a,b,sel;
```

```
wire sel_n,t1,t2;
```

```
not U0(sel_n,sel);  
and U1(t1,a,sel);  
and U2(t2,b,sel_n);  
or U3(out,t1,t2);
```

```
endmodule
```



# Testbench (1/4)

- module testfixture;
  - Declare signals
  - Instantiate modules
  - Applying stimulus
  - Monitor signals
- endmodule

# Testbench (2/4)





- Declare signals
  - Test pattern must be stored in storage elements first and then apply to DUT (Device under Test)
    - Use “**reg**” to declare the storage element
- Instantiate modules
  - Both behavioral level or gate level model can be used.


  
# Testbench (3/4)

- Describing Stimulus

- The testbench always be described behaviorally.
- Procedural blocks are bases of behavioral modeling.
- The simulator starts executing all procedure blocks at time 0 and executes them concurrently.
- Two types of procedural blocks
  - initial
  - always





# Testbench (4/4)

```
• module test_SMUX;
•
•   reg          A,B,SEL;
•   wire         OUT;
•
•   SMUX U0(.out(OUT),.a(A),.b(B),.sel(SEL));
•
•   initial
•   begin
•       A=0;B=0;SEL=0;
•       #10    A=0;B=1;SEL=1;
•       #10    A=1;B=0;
•       #10    SEL=0;
•       .....
•       #10    SEL=1;
•   end
•
•   endmodule
```

**Declare signals**

**Make an instance**

**Assign values to storage elements**

**#10 to specify 10 time unit delay**

**Example: always**

```
initial clk = 0;
always #10 clk = ~clk;
```

```
initial clk=0;
always
begin
clk = 0;
#10;
clk = 1;
#10;
end
```

# Outline

---



- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits

# Verilog HDL Coding Tokens




- Verilog HDL coding tokens
  - White space (空白)
  - Comments (註解)
  - Keyword (關鍵字)
  - Identifier (識別子)
  - Operator (運算子)
  - Number (數字)
  - ....
 
# White Space and Comment



- White space makes code more readable
  - Include blank space (`\b`), tabs (`\t`), and carriage return (`\n`).
- Comments
  - `/* ... */` : mark more than one line
  - `//` : mark only one line.



```
module SMUX(out,a,b,sel);
output    out;
input     a,b,sel;
// The following are logic gates
not       U0(sel_,sel);
and       U1(a1,a,sel_),
          U2(b1,b,sel);
or        U3(out,a1,b1); /* This
                           comment marks more than one
                           line*/
endmodule
```



# Keywords




- Pre-defined non-escaped identifiers that used to define the language construct.
- All keywords are defined in lower cases.
- Examples
  - module, endmodule
  - input, output, inout, wire
  - reg, integer, real, time
  - not, and, or, nand, nor, xor
  - parameter
  - begin, end
  - fork, join, assign
  - always, for, if, else
  - negedge, posedge
- Verilog is a case sensitive language.
  - Use “-u” option in command line option for case-insensitive.


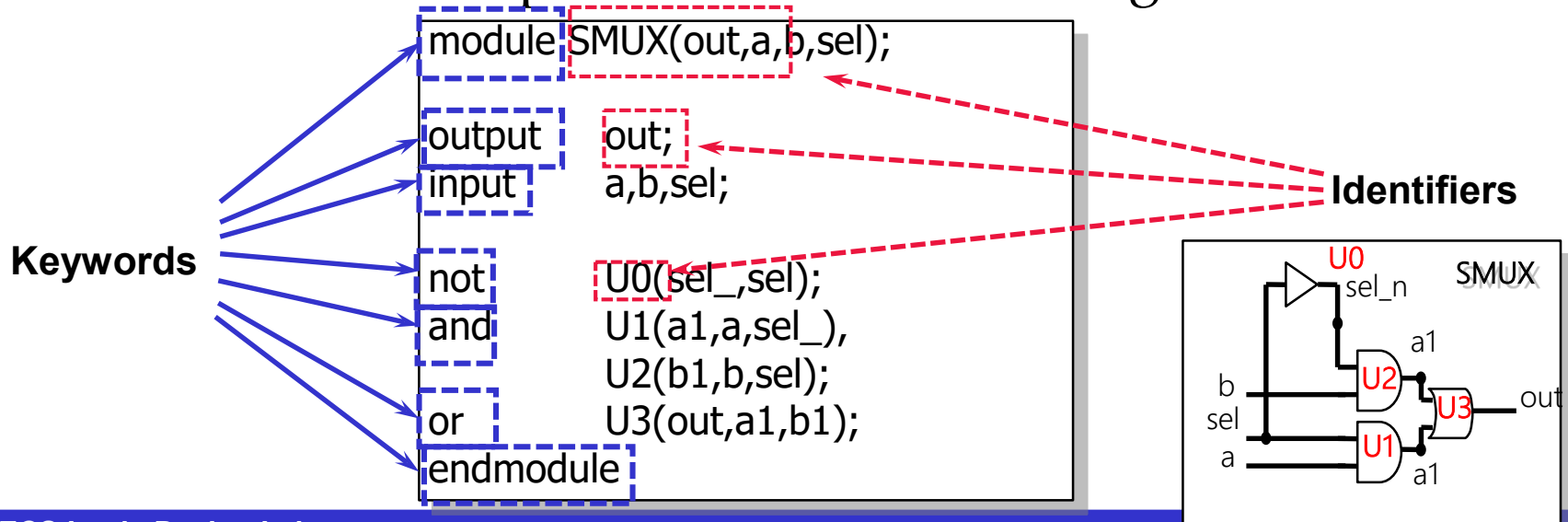
# Identifiers

- Names of modules, ports, and instances are identifiers.
- Identifiers are **user-defined** names for Verilog objects within a description.
- Legal characters in identifiers:
  - a-z, A-Z, 0-9, `_`, `$`
- The **first character of an identifier** must be an **alphabetical character (a-z, A-Z) or an underscore (`_`)**.
- Identifiers can be up to 1023 characters long.






# Operators (1/3)

Bitwise Operators		
OP	Usage	Description
$\sim$	$\sim m$	Invert each bit of m
$\&$	$m \& n$	AND each bit of m with each bit of n
$ $	$m   n$	OR each bit of m with each bit of n
$\wedge$	$m \wedge n$	Exclusive OR each bit of m with n
$\sim\wedge$ or $\wedge\sim$	$m \sim\wedge n$ or $m \wedge\sim n$	Exclusive NOR each bit of m with n

Unary Reduction Operators		
OP	Usage	Description
$\&$	$\&m$	AND all bits in m together (1-bit result)
$\sim\&$	$\sim\&m$	NAND all bits in m together (1-bit result)
$ $	$ m$	OR all bits in m together (1-bit result)
$\sim $	$\sim m$	NOR all bits in m together (1-bit result)
$\wedge$	$\wedge m$	Exclusive OR all bits in m (1-bit result)
$\sim\wedge$ or $\wedge\sim$	$\sim\wedge m$ or $\wedge\sim m$	Exclusive NOR all bits in m (1-bit result)

 

# Operators (2/3)

Arithmetic Operators		
OP	Usage	Description
+	$m + n$	Add n to m
-	$m - n$	Subtract n from m
-	$-m$	Negate m (2's complement)
*	$m * n$	Multiply m by n
/	$m / n$	* Divide m by n
%	$m \% n$	* Modulus of m / n

\* **Synthesis not supported** : The divisor for divide operator may be restricted to constants and a power of 2

Logical Operators		
OP	Usage	Description
!	$!m$	Is m not true? (1-bit True/False result)
&&	$m \&\& n$	Are both m and n true? (1-bit True/False result)
	$m    n$	Are either m or n true? (1-bit True/False result)

Equality Operators (compares logic values of 0 and 1)		
OP	Usage	Description
==	$m == n$	Is m equal to n? (1-bit True/False result)
!=	$m != n$	Is m not equal to n? (1-bit True/False result)

Identity Operators (compares logic values of 0, 1, x, and z)		
OP	Usage	Description
===	$m === n$	* Is m identical to n? (1-bit True/False result)
!==	$m !== n$	* Is m not identical to n? (1-bit True/False result)

**Synthesis not supported**

**Synthesis not supported**



# Operators (3/3)

Relational Operators		
OP	Usage	Description
<	$m < n$	Is m less than n? (1-bit True/False result)
>	$m > n$	Is m greater than n? (1-bit True/False result)
<=	$m \leq n$	Is m less than or equal to n? (True/False result)
>=	$m \geq n$	Is m greater than or equal to n? (True/False result)

Logical Shift Operators		
OP	Usage	Description
<<	$m \ll n$	Shift m left n-times
>>	$m \gg n$	Shift m right n-times

Misc Operators		
OP	Usage	Description
? :	$sel?m:n$	If sel is true, select m: else select n
{ }	$\{m,n\}$	Concatenate m to n, creating larger vector
{ }	$\{n\{m\}\}$	Replicate m n-times

# Integer and Real Numbers



- Numbers can be integer or real numbers.
- Integer can be sized or unsized. Sized integer can be represented as
  - `<size>'<base><value>`
    - size : size in bits
    - base : can be b(binary), o(octal), d(decimal), or h(hexadecimal)
    - value : any legal number in the selected base and x, z, ?.
- Real numbers can be represented in decimal or scientific format.

# Integer and Real Numbers



- 16 : 32 bits decimal
- 8'd16
- 8'h10
- 8'b0001\_0000
- 8'o20
- 32'bx : 32 bits x
- 2'b1? : ? represents a high impedance bit
- 6.3
- 5.3e-4
- 6.2e3

# Concatenation and Replication Operators



- Bit replication for 01010101
  - assign byte = {4{2'b01}};
- Sign extension
  - wire [7:0] byte;
  - assign word = {{8{byte[7]}},byte};





# Input/Output Ports Declaration


- Input/output port declaration
  - **input** : 輸入埠
  - **output** : 輸出埠
  - **inout** : 雙向埠具輸出輸入特性

## Input/Output Ports

```
module MUXS(out,a,b,sel);  
output out;  
input a,b,sel;  
// The following are logic gates  
not U0(sel_,sel);  
and U1(a1,a,sel_),  
U2(b1,b,sel);  
or U3(out,a1,b1);  
endmodule
```
 
## Inout Ports

```
module bidir(rw, din, da, iop);  
input rw, din, da;  
inout iop;  
  
assign iop = rw ? ((din) ? da : iop) : 1'bz;  
  
endmodule
```





# Data Types and I/O Ports

- Verilog basic data types
  - **wire** : 一條接線(只能被動顯示硬體運算結果，無法設定特定值)
  - **wand** : wired AND 接線 (FPGA not support)
  - **wor** : wired OR 接線 (FPGA not support)
  - **reg** : 暫存接線(主要來用來儲存設定特定值)
  - **integer (32-bit signed), real, float, time**: 特性如reg，但只能用於test bench module的運算。
- 使用於所設計的邏輯模組內的通常只有**wire (net property)**與**reg (reg property)**。
- input/output/inout 輸出入埠預設為**wire**的特性。

# Characteristics of reg and wire



- wire

- 資料型態為wire 的變數為連接硬體元件之連接線。
- 變數必須被驅動，才能改變它的內容。
- 除非被宣告為一向量，否則wire 型態的變數內定為一個位元的值，且其內定值為z。
- 使用wire 所宣告的變數必須配合assign 敘述來改變其值，不能在always 區塊中作為敘述的等號左值。





- reg

- 宣告為資料型態reg 之變數的功能和一般程式語言中的變數類似，可以直接給定一個數值。
- 除非被宣告為一向量，否則reg 型態的變數內定為一個位元的值，且其值為X。
- 使用reg 所宣告的變數必須使用在always 區塊中作為敘述的等號左值。


    
# Value Sets

- 4-value logic system in Verilog
  - 0: Logic 0, Zero, False, Ground, Vss, Negative
  - 1: Logic 1, One, True, Power, Vdd, Positive
  - X: Unknown value
  - Z: High Impedance, Floating State, Tri-State, Disable driver.





# Behavior Modeling

- Behavior model concerns only the function of the module without considering the operation of the circuits.
- Verilog is an event-driven timing control language.
  - Events:
    - Value change of reg or wire
    - Value change of input port
  - Synthesizable description of event control
    - Positive edge, negative edge, and value of changes of signals



# always Description

- **always** monitors the change of input signals and update the output signals once the input changes.
  - **begin/end** are used when multiple statements respond to a specific event.

```
always@(event description)  
logic statement;
```

- Event description

- Single signal (level trigger)

```
always@(in1)
```

- Multiple signals (level trigger)

```
always@(in1 or in2 or in3)
```

- Edge trigger event (edge trigger)

```
always@(posedge clk)
```

```
always@(event description)  
begin  
logic statement 1;  
logic statement 2;  
end
```

```
always@(posedge clk or negedge reset)
```



# if or if-else Description

- **if** is a conditional operation that checks the logic value (1 or 0)(true or false) to perform the following statement.
- **if** must be placed inside the **always** statement.
  - If always@(event) is level-triggered, if(expression) is level-triggered.
  - If always@(event) is edge-triggered, if(expression) is edge-triggered.
- **begin/end** are used when multiple statements are determined by a specific expression.

```
if(expression)
statement;
```

```
if(expression)
begin
statement1;
statement2;
end
```

```
if(expression)
statement1_true;
else
statement1_false;
```

```
if(expression)
begin
statement1_true;
statement2_true;
end
else
begin
statement1_false;
statement2_false;
end
```



# case Description

- **case** is a conditional operation that checks multiple cases for perform the multiple statements in a tabular form.
  - If all conditions are stated, it is called “full case”; otherwise, it is not “full case”
  - The **default** case and statement are optional, but should be always included for circuit stability even if it is “full case”.

```
case (signal)
case0: statement0;
case1: statement1;
...
default: def_statement;
endcase
```

```
module decoder(X, out);
input [0:1] X;
output [0:3] out;
reg [0:3] out;
always@(X) begin
case (X)
2'b00: out = 4'b0001;
2'b01: out = 4'b0010;
2'b10: out = 4'b0100;
default: out = 4'b0000;
endcase
end
endmodule
```


```
module decoder(X, out);
input [0:1] X;
output [0:3] out;
reg [0:3] out;
always@(X) begin
case (X)
2'b00: out = 4'b0001;
2'b01: out = 4'b0010;
2'b10: out = 4'b0100;
2'b11: out = 4'b1000
default: out = 4'b0000;→instable
endcase
end
endmodule
```


 
# Example (1/3)

- **Continuous Assignment**
  - `? : ;` Conditional operators (multiplexer)

```
module SMUX(out,a,b,sel);  
output out;  
input a,b,sel;  
  
    assign out = (sel) ? a : b ;  
  
endmodule
```




## Example (2/3)

- **if-else** statements
  - Not for large multiplexers

```
module SMUX(out,a,b,sel)
output out;
input a,b,sel;
reg out;

always @(sel or a or b)
  if (sel)
    out = a;
  else
    out = b ;


endmodule
```

 
 
# Example (3/3)

- **case statements**
  - Usually for large multiplexers

```
module SMUX(out,a,b,sel);  
output out;  
input a,b,sel;  
  
reg output;  
always @(sel or a or b)  
case (sel)  
    1'b0: out = b;  
    1'b1: out = a;  
endcase  
  
endmodule
```





# Declaration of Vectors

- Vector declarations
  - `reg <range> <name> ,...,<name>;`
  - `Wire <range> <name>,...,<name>;`
  - Example
    - `reg [3:0] a,b;`
    - `reg [0:3] c;`
    - `wire [7:0] in1;`
    - `wire [0:7] in2;`



# Bit/Partial Bits Selection

- Bit Selection

```
wire [7:0] a, b, c;  
assign c[0] = a[0] & b[0];
```

- Partial Bits Selection

```
wire [7:0] a, b, c;  
assign c[3:0] = a[5:2] & b[7:4];
```

- Replication

```
wire [7:0] a, b, c;  
assign c = {{2{a[7:6]}},{4{b[2]}}};
```


- Concatenation


```
wire [7:0] a, b, c;  
assign c = {a[3:0],b[5:2]};
```
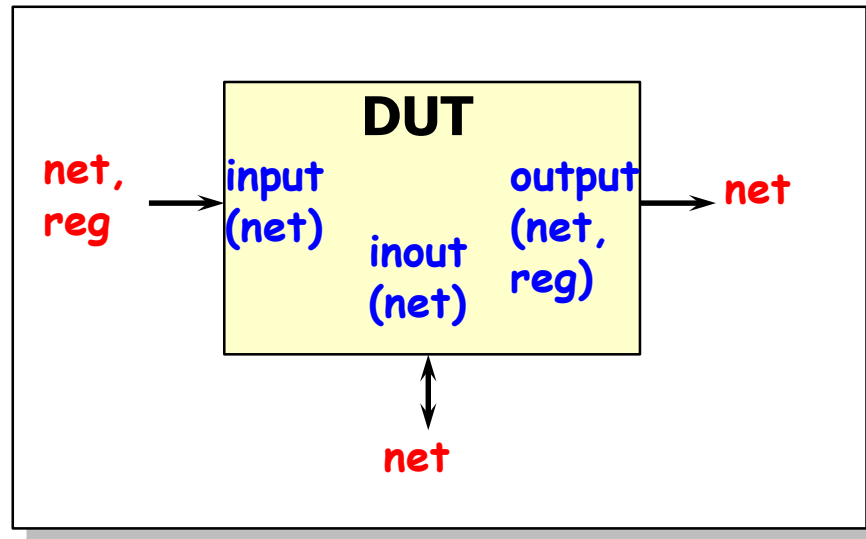
# Port Connection Between Modules



- An **input** or **inout** port must be a net (wire).
- An **output** port can be a register.
- A signal assigned a value in a procedural block (always, initial) must be a register data type.



 

# Common Mistakes in Choosing Data Types

- Make a procedural assignment to a net
  - wire [7:0] databus;
  - always @(read or addr) databus=read ? mem[addr] : 'bz;
  - **Illegal left-hand-side assignment**
- Connect a register to an instance output
  - reg myreg;
  - and (myreg, net1, net2);
  - **Illegal output port specification**
- Declare a module **input** port as a register
  - input myinput;
  - reg myinput;
  - **Incompatible declaration**



# Procedural Assignments

```
module assignment_test;  
reg [3:0] a,b;  
wire [4:0] sum1;  
reg [4:0] sum2;
```

```
assign sum1 = a + b ;
```

```
initial  
begin
```

```
    a=4'b1010;b=4'b0110;
```

```
    sum2 = a + b;
```

```
    $display("a b sum1 sum2");
```

```
    $monitor(a,b,sum1,sum2);
```

```
    #10 a=4'b0001;
```

```
end
```

```
endmodule
```

Continuous assignment

Procedural assignment

```
module FA(s,co,a,b,ci);  
input a,b,ci;  
output s,co;  
reg s;
```

```
s=a^b^ci;
```

```
always @(a or b or ci)  
begin
```

```
    assign co=(a&b)|(b&ci)|(a&ci);
```

```
end
```

```
endmodule
```

Error! Illegal left-hand-side  
continuous assignment.

Error! Illegal left-hand-side  
in assign statement.





# Parameter

- parameter敘述可用於定義一個常數供模組用來定義輸出入埠的寬度、向量的大小等
  - parameter name = number;

```
module add8(a, b, c);  
parameter width=8;  
input [width-1:0] a, b;  
output [width-1:0] c;  
  
assign c = a + b;  
  
endmodule
```



# Compiler Directives

- Verilog 語言跟 C 語言一樣提供編譯命令 (compiler directives) 供使用者利用，指示編譯程式進行編譯的前置作業。

- ``define`
- ``include`

```
`define LEN 4
module buf4(in, out, clock);
input  [`LEN-1:0] in;
input  clock;
output [`LEN-1:0] out;
reg    [`LEN-1:0] out;
...
```

fa1.v

```
module fa1(a, b, ci, s, co);
input  a, b, ci;
output s, co;
assign {co, s} = a + b + ci;
endmodule
```

fa2.v

```
`include "fa1.v"
module fa2(a, b, ci, s, co);
input  [1:0] a, b;
input  ci;
output [1:0] s;
output co;
wire   c1;
fa1 fa0(a[0],b[0],ci,s[0],c1);
fa1 fa1(a[1],b[1],c1,s[1],co);
endmodule
```

- ``define` 用來定義模組中使用到的常數。
- ``include` 用來引入其他verilog檔案一起編譯與合成。
- 如果已經在proj list已經都加入fa1.v fa2.v，就沒有必要使用 ``include fa1.v`



# Module Connections

- Module connection can be called by **port order** or **port names**.
- **call-by-name** can ignore the port order defined in the module.

```
module ha(a,b,sum,co)
input a,b;
output sum,co;
wire sum,co;
assign sum = a^b;
assign co=a&b;
endmodule
```

## call by port order

```
module adder(a_in,b_in,sum_out,carry_cout)
input a_in,b_in;
output sum_out,co_out;
wire sum_out,co_out;
ha adder0(a_in,b_in,sum_out,carry_out);
endmodule
```

## call by port names

```
module adder(a_in,b_in,sum_out,carry_cout)
input a_in,b_in;
output sum_out,co_out;
wire sum_out,co_out;
ha adder0(.b(b_in),
           .a(a_in),
           .sum(sum_out),
           .co(carry_out));
endmodule
```

# Outline

---




- Introduction
- Verilog Modules
- Verilog HDL Coding
- Examples of Combinational Circuits


 
# MUX 1

```
module mux(  
    out, // output  
    a, // input a  
    b, // input b  
    c, // input c  
    d, // input d  
    sel // selection control signal  
);  
  
output out; // output  
input a; // input a  
input b; // input b  
input c; // input c  
input d; // input d  
input [1:0] sel; // selection control signal  
reg out; // output (in always block)  
  
always @(sel or a or b or c or d)  
    if (sel==2'b00) out = a;  
    else if (sel==2'b01) out = b;  
    else if (sel==2'b10) out=c;  
    else out=d;  
endmodule
```




Final "else ---;" is required


 
# MUX 2

```
module mux(  
    out, // output  
    a, // input a  
    b, // input b  
    c, // input c  
    d, // input d  
    sel // selection control signal  
);  
  
output out; // output  
input a; // input a  
input b; // input b  
input c; // input c  
input d; // input d  
input [1:0] sel; // selection control signal  
reg out; // output (in always block)  
  
always @(sel or a or b or c or d)  
    case (sel)  
        2'b00: out = a;  
        2'b01: out = b;  
        2'b10: out = c;  
        2'b11: out = d;  
        default: out = 0;  
    endcase  
endmodule
```



Final "default : ---;" is required




# Design Procedure

- 1 • From the *specifications*, determine the inputs, outputs, and their symbols.
- 2 • Derive the *truth table (functions)* from the relationship between the inputs and outputs
- 3 • Derive the *simplified Boolean functions* for each output function.
- 4 • Draw the logic diagram.
- 5 • Construct the Verilog code according to the logic diagram.
- 6 • Write the testbench and verify the design.


 
# Seven-Segment Display Decoder (1/2)



1 input:  $bcd[3:0]$   
output:  $display[7:0]$



2

  

3

BCD  $\rightarrow$  7-segment\_star\_dot

0000  $\rightarrow$  0000001\_1

0001  $\rightarrow$  1001111\_1

0010  $\rightarrow$  0010010\_1

0011  $\rightarrow$  0000110\_1

0100  $\rightarrow$  1001100\_1

0101  $\rightarrow$  0100100\_1

0110  $\rightarrow$  0100000\_1

0111  $\rightarrow$  0001111\_1

1000  $\rightarrow$  0000000\_1

1001  $\rightarrow$  0000100\_1

others  $\rightarrow$  0111000\_1 (F)

4





# Seven-Segment Display Decoder (2/2)



5

```
module ssd(
    display, // SSD display output
    bcd // BCD input
);

output [7:0] display; // SSD display output
input [3:0] bcd; // BCD input

reg [7:0] display; // SSD display output (in always)


// Combinational logics:
always @(bcd)
    case (bcd)
        4'd0: display = 8'b 0000001_1; //0
        4'd1: display = 8'b 1001111_1; //1
        4'd2: display = 8'b 0010010_1; //2
        4'd3: display = 8'b 0000110_1; //3
        4'd4: display = 8'b 1001100_1; //4
        4'd5: display = 8'b 0100100_1; //5
        4'd6: display = 8'b 0100000_1; //6
        4'd7: display = 8'b 0001111_1; //7
        4'd8: display = 8'b 0000000_1; //8
        4'd9: display = 8'b 0000100_1; //9
        default: display = 8'b 0111000_1 ; //F
    endcase

endmodule
```

 
# 2-bit Absolute Value Calculator (1/3)




1 input:  $z[1:0]$   
output:  $z\_abs[2:0]$



 2 If  $z$  is negative (MSB is 1), complement every bit and add 1.  
If  $z$  is positive (MSB is 0), output remains the same as input.  
Use XOR for MSB and every bit.



# 2-bit Absolute Value Calculator (2/3)

 

module : abs.v

5

```
module abs(  
  z_abs, // absolute value of z  
  z // original value  
);  
  
output [2:0] z_abs; // absolute value of z  
input [1:0] z; // original value  
  
reg [1:0] z_tmp; // XOR output  
reg [2:0] z_abs; // register for Z  
  
// Combinational logics:  
always @(z)  
begin  
  z_tmp[1]=z[1]^z[1];  
  z_tmp[0]=z[0]^z[1];  
  z_abs={z_tmp[1],z_tmp[0]}+{2'b0,z[1]};  
end  
  
endmodule
```

testbench module : t\_abs.v

6

```
module t_abs;  
  
wire [2:0] z_abs; // absolute value of z  
reg [1:0] z; // original value  
  
abs U0(.z_abs(z_abs),.z(z));  
  
initial  
begin  
  z=2'b00;  
  #5 z=2'b01;  
  #5 z=2'b10;  
  #5 z=2'b11;  
  #5 z=2'b00;  
end  
  
endmodule
```

# 2-bit Absolute Value Calculator (3/3)

