

Lab 4 - Counters and Shifters II

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

2022-03-28

Contents

Lab 4 - Counters and Shifters II Report	4
Lab 4 - 1: 1Hz 4-bit Synchronous Binary Down Counter	4
Design Specification	4
Design Implementation	4
Frequency Divider	4
4-bit Synchronous Binary Down Counter	5
1 Hz 4-bit Synchronous Binary Down Counter	6
I/O Pin Assignment	7
Block Diagram	7
RTL Simulation	8
Lab 4 - 2: 1Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display	8
Design Specification	8
Design Implementation	9
Frequency Divider	9
4-bit Synchronous Binary Down Counter	9
1 Hz 4-bit Synchronous Binary Down Counter	9
Binary to 7-Segment Display	9
1 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display	10
I/O Pin Assignment	10
Block Diagram	11
RTL Simulation	11
Lab 4 - 3: 0.5Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display	11
Design Specification	11
Frequency Divider	11
Design Implementation	12
Frequency Divider	12
4-bit Synchronous Binary Down Counter	13
1 Hz 4-bit Synchronous Binary Down Counter	13
Binary to 7-Segment Display	13
0.5 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display	13
I/O Pin Assignment	14
Block Diagram	15
RTL Simulation	15
Lab 4 - 4: 1Hz 8-bit Synchronous Binary Up Counter To 7-Segment Display	15
Design Specification	15

Design Implementation	16
Frequency Divider	16
8-bit Synchronous Binary Up Counter	16
1Hz 8-bit Synchronous Binary Up Counter	16
Extractor	17
Binary to 7-Segment Display	17
7-Segment Display Controller	17
1Hz 8-bit Synchronous Binary Up Counter To 7-Segment Display	19
I/O Pin Assignment	20
Block Diagram	20
RTL Simulation	21
Discussion	21
Conclusion	21
Reference	21

Lab 4 - Counters and Shifters II Report

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

Lab 4 - 1: 1Hz 4-bit Synchronous Binary Down Counter

Design Specification

Source Code

Frequency Divider

Input: rst, clk

Output: clk_out

4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

1Hz 4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

Design Implementation

Frequency Divider To generate the 1 Hz clock, I use variables counter_in and counter_out to count from 0 to 50M. The counter_in will store the value for the next time step and pass the value to the counter_out when the clock raises. The reason why we need 50M counting is each counting is triggered only when the clock raises, so the circuit will count 1 more for every twice clock pulses.

```
1 `define FREQ_DIV_BITS 30
2 //`define FREQ_DIV_COUNT `FREQ_DIV_BITS'd10000000
3 `define FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000000
4
5 module frequency_divider(
6     clk_out,
7     // counter,
8     clk,
9     rst
```

```
10 );
11
12 input clk;
13 input rst;
14 output clk_out;
15 // output counter;
16
17 reg clk_in;
18 reg clk_out;
19 reg [`FREQ_DIV_BITS-1:0] counter_in;
20 reg [`FREQ_DIV_BITS-1:0] counter_out;
21
22 always@(counter_out or clk_out)
23     if(counter_out < (`FREQ_DIV_COUNT - 1))
24     begin
25         counter_in <= counter_out + `FREQ_DIV_BITS'd1;
26         clk_in <= clk_out;
27     end
28     else
29     begin
30         counter_in <= `FREQ_DIV_BITS'd0;
31         clk_in <= ~clk_out;
32     end
33
34 always@(posedge clk or negedge rst)
35     if(~rst)
36     begin
37         counter_out <= `FREQ_DIV_BITS'd0;
38         clk_out <= 1'd0;
39     end
40     else
41     begin
42         counter_out <= counter_in;
43         clk_out <= clk_in;
44     end
45 endmodule
```

4-bit Synchronous Binary Down Counter To implement the binary down counter, I use a variable q_in to count from 0 to 15. Whenever the output of the counter q changes, the variable q_in should be changed to $q - 1$. In addition, when the circuit detects the raise of the clock, the output of the counter will change to the variable q_in . On the other hand, if the reset switch to 0 or the counter hits 0, q will be reset to the upper limit 15.

Verilog Code

```
1 `define BCD_COUNTER_BITS 4
2
3 module binary_down_counter(
```

```

4      q,
5      clk,
6      rst
7  );
8
9      output [`BCD_COUNTER_BITS-1:0]q;
10     input clk;
11     input rst;
12
13     reg [`BCD_COUNTER_BITS-1:0]q;
14     reg [`BCD_COUNTER_BITS-1:0]q_in;
15
16     always@(q)
17     begin
18         q_in <= q - `BCD_COUNTER_BITS'd1;
19     end
20
21     always@(posedge clk or negedge rst)
22     begin
23         if(~rst)
24             begin
25                 q <= `BCD_COUNTER_BITS'd0;
26             end
27         else
28             begin
29                 q <= q_in;
30             end
31     end
32 endmodule

```

1 Hz 4-bit Synchronous Binary Down Counter All we need to do is combine the 1 Hz frequency divider and the 4-bit binary down counter which triggered by the 1 Hz frequency divider.

```

1  `define BCD_COUNTER_BITS 4
2  `define RST_HIGH 1'b1
3
4  module lab4_1(
5      q,
6      rst,
7      clk
8  );
9      output [`BCD_COUNTER_BITS-1:0]q;
10     input rst;
11     input clk;
12
13     // reg [`BCD_COUNTER_BITS-1:0]q;
14     wire DIV_CLK;
15
16     frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));

```

```

17     binary_down_counter U1(.clk(DIV_CLK), .rst(rst), .q(q));
18 endmodule

```

I/O Pin Assignment

I/O	clk	rst	q[0]	q[1]	q[2]	q[3]
LOC	W5	V17	U16	E19	U19	V19

Block Diagram

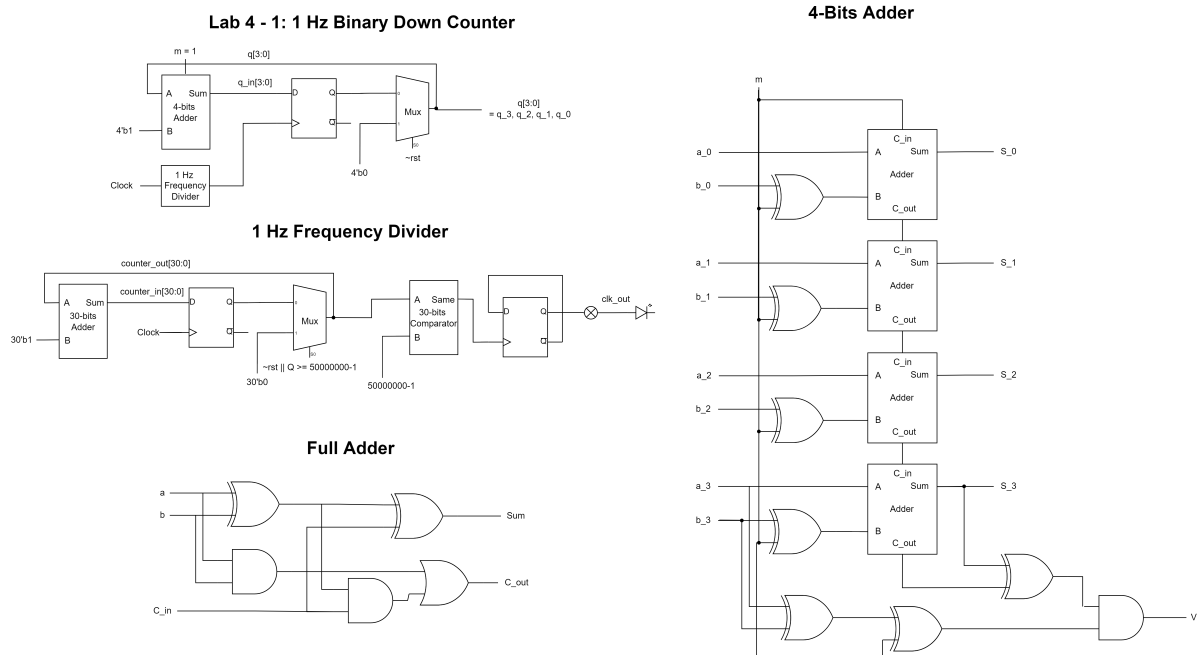
 


Figure 1: Lab 4-1 Logic Diagram

RTL Simulation**Figure 2:** Lab 4-1 RTL Simulation**Lab 4 - 2: 1Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display****Design Specification**

Source Code

Frequency Divider

Input: rst, clk

Output: clk_out

4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

1 Hz 4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

Binary to 7-Segment Display

Input [3:0] i

Output [3:0]P, [7:0]D

1 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

Input rst, clk

Output [3:0]q, [3:0]P, [7:0]D

Design Implementation

Frequency Divider Same as lab 4-1.

4-bit Synchronous Binary Down Counter Same as lab 4-1.

1 Hz 4-bit Synchronous Binary Down Counter Same as lab 4-1.

Binary to 7-Segment Display Convert 4-bit binary number to 7-segment display with switch-case syntax.

```

1  `define INPUT_BITS_N 4
2  `define SEGMENT_7_DISPALY_DIGIT_N 4
3  `define SEGMENT_7_SEGMENT_N 8
4
5  module segment7(
6      input [`INPUT_BITS_N:0] i,
7      output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]P,
8      output [`SEGMENT_7_SEGMENT_N-1:0]D
9  );
10
11     reg [`SEGMENT_7_SEGMENT_N-1:0]D;
12
13     assign P = ~4'b0001;
14     always@(i)
15         case(i)
16             4'd0: D=`SEGMENT_7_SEGMENT_N'b0000001_1;
17             4'd1: D=`SEGMENT_7_SEGMENT_N'b1001111_1;
18             4'd2: D=`SEGMENT_7_SEGMENT_N'b0010010_1;
19             4'd3: D=`SEGMENT_7_SEGMENT_N'b0000110_1;
20             4'd4: D=`SEGMENT_7_SEGMENT_N'b1001100_1;
21             4'd5: D=`SEGMENT_7_SEGMENT_N'b0100100_1;
22             4'd6: D=`SEGMENT_7_SEGMENT_N'b0100000_1;
23             4'd7: D=`SEGMENT_7_SEGMENT_N'b0001111_1;
24             4'd8: D=`SEGMENT_7_SEGMENT_N'b0000000_1;
25             4'd9: D=`SEGMENT_7_SEGMENT_N'b0000100_1;
26             4'd10: D=`SEGMENT_7_SEGMENT_N'b0001000_1;
27             4'd11: D=`SEGMENT_7_SEGMENT_N'b1100000_1;
28             4'd12: D=`SEGMENT_7_SEGMENT_N'b0110001_1;
29             4'd13: D=`SEGMENT_7_SEGMENT_N'b1000010_1;
30             4'd14: D=`SEGMENT_7_SEGMENT_N'b0110000_1;
31             4'd15: D=`SEGMENT_7_SEGMENT_N'b0111000_1;
32             default: D=`SEGMENT_7_SEGMENT_N'b0111000_1;
33         endcase
34
35     endmodule

```

1 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display It's a simple module and just use the divided clock from frequency divider to trigger the binary down counter. The counting of the down counter will be shown in 7-segment display.

```

1  `define BCD_COUNTER_BITS 4
2  `define RST_HIGH 1'b1
3  `define SEGMENT_7_DISPALY_DIGIT_N 4
4  `define SEGMENT_7_SEGMENT_N 8
5
6  module lab4_2(
7      q,
8      P,
9      D,
10     rst,
11     clk
12 );
13     output [`BCD_COUNTER_BITS-1:0]q;
14     output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]P;
15     output [`SEGMENT_7_SEGMENT_N-1:0]D;
16     input rst;
17     input clk;
18
19     // reg [`BCD_COUNTER_BITS-1:0]q;
20     wire DIV_CLK;
21
22     assign P = 4'b1110;
23
24     frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));
25     binary_down_counter U1(.clk(DIV_CLK), .rst(rst), .q(q));
26     segment7 U2(.i(q), .P(P), .D(D));
27 endmodule

```

I/O Pin Assignment

I/O	clk	rst	q[0]	q[1]	q[2]	q[3]	P[0]	P[1]	P[2]	P[3]
LOC	W5	V17	U16	E19	U19	V19	U2	U4	V4	W4

I/O	D[0]	D[1]	D[2]	D[3]	D[4]	D[5]	D[6]	D[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

Block Diagram

Lab 4 - 2: 1 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

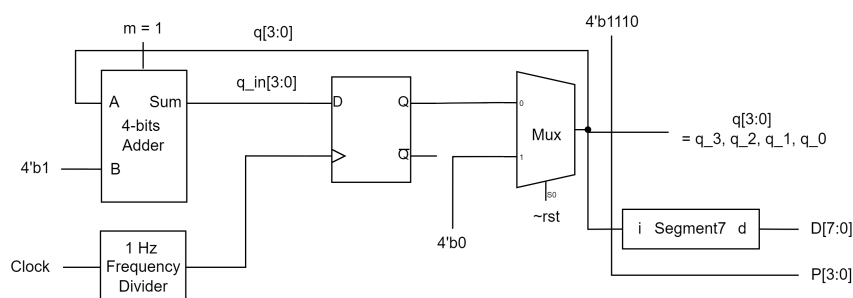


Figure 3: Lab 4-2 Logic Diagram

RTL Simulation

 


Figure 4: Lab 4-2 RTL Simulation

Lab 4 - 3: 0.5Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

Design Specification

Source Code

Frequency Divider Input: rst, clk

Output: clk_out

4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

0.5 Hz 4-bit Synchronous Binary Down Counter

Input: rst, clk

Output [3:0]q

Binary to 7-Segment Display

Input [3:0] i

Output [3:0]P, [7:0]D

0.5 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

Input rst, clk

Output [3:0]q, [3:0]P, [7:0]D

Design Implementation

Frequency Divider It's similar to lab 4-2. I only modify the upper limit of the counter to 100M, which means twice divide the frequency.

```
1  `define  FREQ_DIV_BITS 30
2  //`define  FREQ_DIV_COUNT `FREQ_DIV_BITS'd10000000
3  //`define  FREQ_DIV_COUNT `FREQ_DIV_BITS'd500000000
4  `define  FREQ_DIV_COUNT `FREQ_DIV_BITS'd1000000000
5
6  module frequency_divider(
7      clk_out,
8      clk,
9      rst
10 );
11
12     input clk;
13     input rst;
14     output clk_out;
15
16     reg clk_in;
17     reg clk_out;
18     reg [`FREQ_DIV_BITS-1:0] counter_in;
19     reg [`FREQ_DIV_BITS-1:0] counter_out;
20
21     always@(counter_out or clk_out)
22         if(counter_out < (`FREQ_DIV_COUNT - 1))
```

```

23     begin
24         counter_in <= counter_out + `FREQ_DIV_BITS'd1;
25         clk_in <= clk_out;
26     end
27     else
28     begin
29         counter_in <= `FREQ_DIV_BITS'd0;
30         clk_in <= ~clk_out;
31     end
32
33     always@(posedge clk or negedge rst)
34     if(~rst)
35     begin
36         counter_out <= `FREQ_DIV_BITS'd0;
37         clk_out <= 1'd0;
38     end
39     else
40     begin
41         counter_out <= counter_in;
42         clk_out <= clk_in;
43     end
44 endmodule

```

4-bit Synchronous Binary Down Counter Same as lab 4-1.

1 Hz 4-bit Synchronous Binary Down Counter Same as lab 4-1.

Binary to 7-Segment Display Same as lab 4-1.

0.5 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display We simply combine the previous 3 modules and we can implement the 0.5 Hz binary down counter and show the counting number on the 7-segment display.

```

1  `define BCD_COUNTER_BITS 4
2  `define RST_HIGH 1'b1
3  `define SEGMENT_7_DISPALY_DIGIT_N 4
4  `define SEGMENT_7_SEGMENT_N 8
5
6  module lab4_3(
7      q,
8      P,
9      D,
10     rst,
11     clk
12 );

```

```

13     output [`BCD_COUNTER_BITS-1:0]q;
14     output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]P;
15     output [`SEGMENT_7_SEGMENT_N-1:0]D;
16     input  rst;
17     input  clk;
18
19     //     reg [`BCD_COUNTER_BITS-1:0]q;
20     wire DIV_CLK;
21
22     assign P = 4'b1110;
23
24     frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));
25     binary_down_1digit_counter U1(.clk(DIV_CLK), .rst(rst), .q(q));
26     segment7 U2(.i(q), .P(P), .D(D));
27 endmodule

```

I/O Pin Assignment

I/O	clk	rst	q[0]	q[1]	q[2]	q[3]	P[0]	P[1]	P[2]	P[3]
LOC	W5	V17	U16	E19	U19	V19	U2	U4	V4	W4

I/O	D[0]	D[1]	D[2]	D[3]	D[4]	D[5]	D[6]	D[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

Block Diagram

Lab 4 - 3: 0.5 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

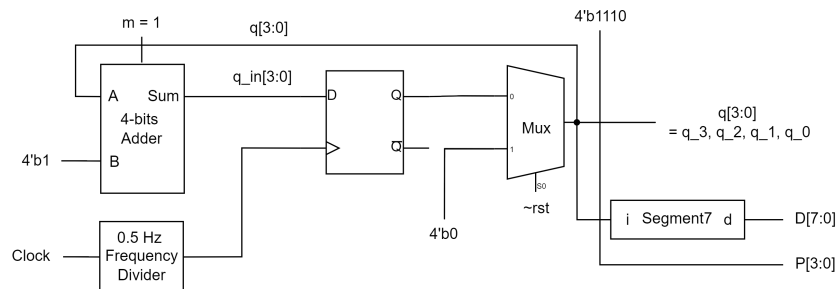


Figure 5: Lab 4-3 Logic Diagram

RTL Simulation

 


Figure 6: Lab 4-3 RTL Simulation

Lab 4 - 4: 1Hz 8-bit Synchronous Binary Up Counter To 7-Segment Display

Design Specification

Source Code

Frequency Divider

Input: rst, clk

Output: clk_out

8-bit Synchronous Binary Up Counter

Input: rst, clk

Output [7:0]q

1Hz 8-bit Synchronous Binary Up Counter

Input: rst, clk

Output [7:0]q

Extractor

Input [7:0] x

Output [3:0] d1, [3:0] d2

Binary to 7-Segment Display

Input [3:0] i

Output [3:0]P, [7:0]D

7-Segment Display

Output [0:3]d_sel, [7:0]d_out

Input clk, rst, [7:0]d0, [7:0]d1, [7:0]d2, [7:0]d3

1Hz 8-bit Synchronous Binary Up Counter To 7-Segment Display

Input rst, clk

Output [3:0]q, [3:0]P, [7:0]D

Design Implementation

Frequency Divider Same as lab 4-1.

8-bit Synchronous Binary Up Counter It's similar to the 4-bit binary down counter in lab 4-1. I only extend the bits array of the counter to 8 bits and use plus 1 instead of minus 1.

1Hz 8-bit Synchronous Binary Up Counter It's similar to the 1 Hz 4-bit binary down counter in lab 4-1. I only extend the bits array of the counter to 8 bits and use plus 1 instead of minus 1.

Extractor I use mod of 10 to extract the first decimal digit and use divided by 10 to extract the second decimal digit.

```

1 module extract(
2     input [7:0] x,
3     output [3:0] d1,
4     output [3:0] d2
5 );
6
7 wire [7:0] mod;
8 wire [7:0] div;
9 assign mod = x % 10;
10 assign div = x / 10;
11
12 assign d1 = mod[3:0];
13 assign d2 = div[3:0];
14 endmodule

```

Binary to 7-Segment Display Same as lab 4-1.

7-Segment Display Controller Since we can only control one digit of the 7-segment display each time, I design a module that takes the 4-digit patterns as input and shows the 1 digit on the display when the clock raises. Whenever the clock raises, the module will switch the control d_sel to different digit and shows the corresponding digit. Take an example, when the first clock raise occur, the module will set d_sel = 4' b1110 and d_out = d0. As for second clock pulse, the module will output d_sel = 4' b1101 and d_out = d1 and so on.

```

1 `define DIGIT_N 4
2 `define SEGMENT_N 8
3 `define NONE_BITS `SEGMENT_N'b1111111_0
4 `define EMPTY_BITS `SEGMENT_N'b1111111_1
5
6 module display_7seg(
7     d_sel,
8     d_out,
9     clk,
10    rst,
11    d0,
12    d1,
13    d2,
14    d3
15 );
16
17 output [0:`DIGIT_N-1] d_sel;
18 output [`SEGMENT_N-1:0] d_out;
19 input clk;

```

```
20     input rst;
21     input [`SEGMENT_N-1:0]d0;
22     input [`SEGMENT_N-1:0]d1;
23     input [`SEGMENT_N-1:0]d2;
24     input [`SEGMENT_N-1:0]d3;
25
26     reg [0:`DIGIT_N-1]d_sel;
27     reg [`SEGMENT_N-1:0]d_out;
28     reg [0:`DIGIT_N-1]d_sel_temp;
29     reg [`SEGMENT_N-1:0]d_out_temp;
30     wire clk_out;
31
32     // initial
33     // begin
34     //     d_sel_temp <= `DIGIT_N'b1110;
35     //     d_out_temp <= `EMPTY_BITS;
36     // end
37
38     segment7_frequency_divider U0(.clk(clk), .rst(rst), .clk_out(
        clk_out));
39
40     always@(d_sel)
41     begin
42         case((d_sel << 1) | (d_sel >> (`DIGIT_N-1)))
43             `DIGIT_N'b1110: d_out_temp <= d0;
44             `DIGIT_N'b1101: d_out_temp <= d1;
45             `DIGIT_N'b1011: d_out_temp <= d2;
46             `DIGIT_N'b0111: d_out_temp <= d3;
47             default: d_out_temp <= `NONE_BITS;
48         endcase
49         d_sel_temp <= (d_sel << 1) | (d_sel >> (`DIGIT_N-1));
50     end
51
52     always@(posedge clk_out or negedge rst)
53     begin
54         if(~rst)
55         begin
56             d_out <= `EMPTY_BITS;
57             d_sel <= `DIGIT_N'b1110;
58         end
59         else
60         begin
61             d_out <= d_out_temp;
62             d_sel <= d_sel_temp;
63         end
64     end
65
66 endmodule
```

1Hz 8-bit Synchronous Binary Up Counter To 7-Segment Display I combine the all modules mentioned above. First, I generate a 1 Hz clock to trigger the 8-bit up counter and output the number of counting. Then, extract the both decimal digits of the binary number of counting. Finally, show the decimal digits on the 7-segment display.

```

1  `define BCD_COUNTER_BITS 8
2  `define RST_HIGH 1'b1
3
4  `define INPUT_BITS_N 4
5  `define SEGMENT_7_DISPALY_DIGIT_N 4
6  `define SEGMENT_7_SEGMENT_N 8
7
8  `define P 4'b1111
9  `define NONE_SEG7 `SEGMENT_7_SEGMENT_N'b1111111_1
10
11 module lab4_4(
12     q,
13     D_SEL,
14     D_OUT,
15     rst,
16     clk
17 );
18     output [`BCD_COUNTER_BITS-1:0]q;
19     output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]D_SEL;
20     output [`SEGMENT_7_SEGMENT_N-1:0]D_OUT;
21     input rst;
22     input clk;
23
24     // reg [`BCD_COUNTER_BITS-1:0]q;
25     wire DIV_CLK;
26     wire [`INPUT_BITS_N-1:0]D1_BINARY;
27     wire [`INPUT_BITS_N-1:0]D2_BINARY;
28     wire [`SEGMENT_7_SEGMENT_N-1:0]D1_SEGMENT7;
29     wire [`SEGMENT_7_SEGMENT_N-1:0]D2_SEGMENT7;
30
31     // 2-Digits Binary up counter
32     frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));
33     binary_up_2digit_counter U1(.clk(DIV_CLK), .rst(rst), .q(q));
34
35     // Extract digits
36     extract U2(.x(q), .d1(D1_BINARY), .d2(D2_BINARY));
37
38     // Convert binary to 7-segment
39     segment7 U3(.i(D1_BINARY), .D(D1_SEGMENT7));
40     segment7 U4(.i(D2_BINARY), .D(D2_SEGMENT7));
41
42     // Show
43     display_7seg U5(.clk(clk), .rst(rst), .d0(D1_SEGMENT7), .d1(
        D2_SEGMENT7), .d2(`NONE_SEG7), .d3(`NONE_SEG7), .d_sel(D_SEL), .
        d_out(D_OUT));

```

44 **endmodule**

I/O Pin Assignment

I/O	clk	rst	q[0]	q[1]	q[2]	q[3]	P[0]	P[1]	P[2]	P[3]
LOC	W5	V17	U16	E19	U19	V19	U2	U4	V4	W4

I/O	D[0]	D[1]	D[2]	D[3]	D[4]	D[5]	D[6]	D[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

Block Diagram

Lab 4 - 4: 1 Hz 4-bit Synchronous Binary Down Counter To 7-Segment Display

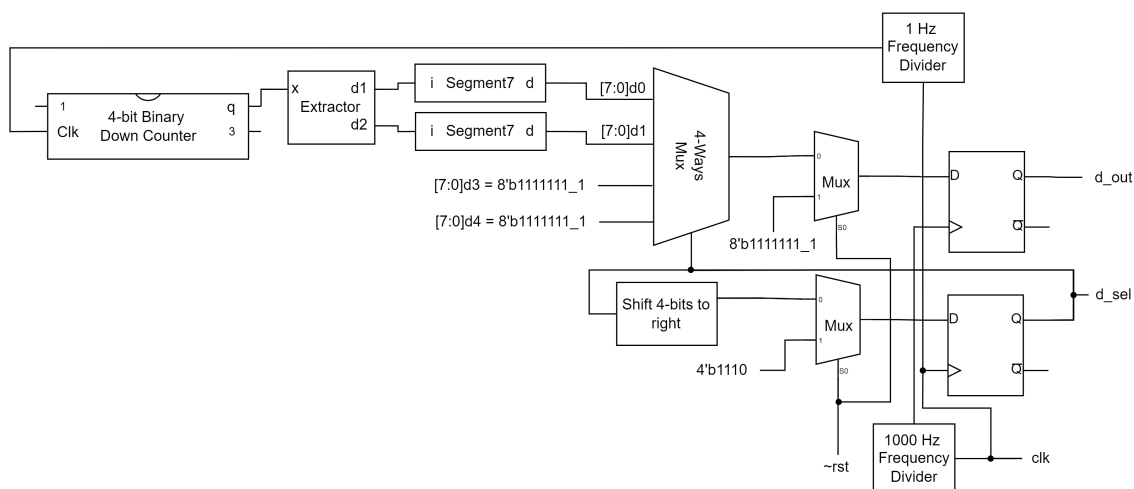


Figure 7: Lab 4-4 Logic Diagram

RTL Simulation

 


Figure 8: Lab 4-4 RTL Simulation

Discussion

In lab 3-5, first I use 100M Hz clock to trigger the 7-segment display to switch the controlling digits and it doesn't work. As a result, I gradually slower down the update frequency to 1000 Hz(which is divided by 50000×2) and the module "7-Segment Display Controller" finally worked. In lab4-4, I use the same module. In addition, in lab 4-3 I divided the 100M Hz clock with 25M and I got wrong clock frequency because it would provide 2 Hz clock. Then, I divided the 1 Hz clock with 100M and got 0.5 Hz clock.

Conclusion

The lab4 seems like an extension of the lab3. However, we've still learned additional sequential logic circuit, including frequency divider and binary down counter etc...Thanks for lab4, I will be more familiar with the sequential logic design.

Reference

- None