



Verilog HDL – II

Sequential Logics

黃元豪

Yuan-Hao Huang

國立清華大學電機工程學系

Department of Electrical Engineering
National Tsing-Hua University

Outline

- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits



Sequential Logic Circuits




- Memory Devices
 - Latch
 - Flip-flop
 - Register
- Sequential Circuits
 - Synchronous Counters
 - General Synchronous Sequential Circuits
- Finite State Machine
 - Moore Machine
 - Mealy Machine



Latch

- Latch is an level-triggered storage with a trigger signal enable.
- It is suggested not to use the level-triggering latch in the experiment.
 - Transparent Q
 
```
module latch_d(Enable, D, Q);  
  input Enable, D;  
  output Q;  
  reg Q;  
  
  always@(Enable or D)  
    if (Enable)  
      Q = D;  
  
endmodule
```



Flip-Flop

- Flip-flop with synchronous clock and asynchronous reset
 - Opaque flip-flop

```





module D_FF_SR(clock, reset, D, Q);
input  clock, reset, D;
output Q;
reg   Q;

```

```

always @(posedge clock or negedge reset)
begin
if (reset == 1'b0)
Q = 1'b0; // reset
else
Q = D;
end

```

    





Register

- 16-bit synchronous register with clear
 
```
module reg_16(clear, clock, in, out);  
  input  clear, clock;  
  input  [0:15] in;  
  output [0:15] out;  
  reg    [0:15] out;  
  
  always@(posedge clock or posedge clear)  
  begin  
    if (clear == 1'b1)  
      out = 16'b0;  
    else out = in;  
  end  
endmodule
```



 

Synchronous Counter

- It is recommended that the logic circuits and the flip-flops are coded separately.

Logic circuits and flip-flops are jointly coded.

```
module counter1(direct, clk, reset, out);
input  direct, clk, reset;
output [0:3] out;
reg    [0:3] out;

always@(posedge clk or negedge reset) begin
if (~reset)
out <= 4'b0000;
else
begin
if (direct)
out <= out + 1;
else
out <= out -1;
end
end
endmodule
```

Logic circuits and flip-flops are separately coded.

```
module counter1(direct, clk, reset, out);
input  direct, clk, reset;
output [0:3] out;
reg    [0:3] out;
wire   [0:3] out_temp;


// Logic circuits
assign out_temp = (direct) ? out+1 : out-1;

// Flip-flops
always@(posedge clk or negedge reset) begin
if(~reset)
out <= 4'b0000;
else
out <= out_temp;
end

endmodule
```

Generalized Sequential Circuits

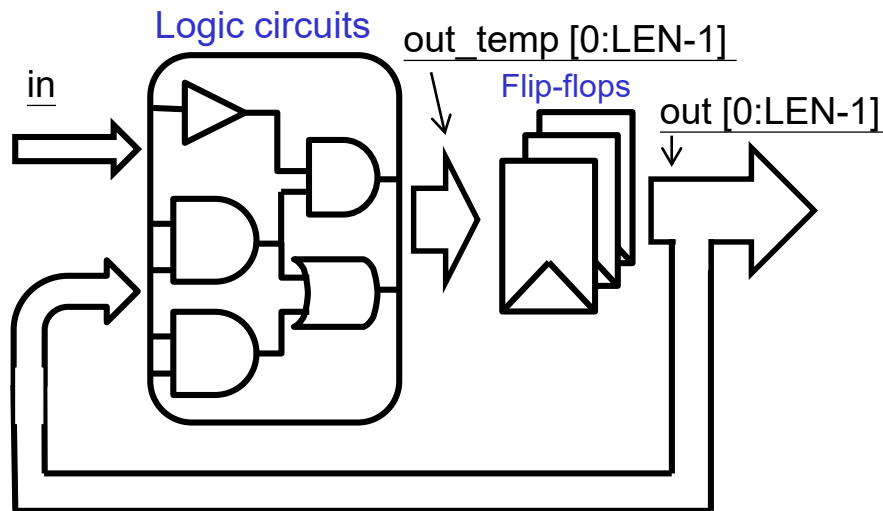- Recommended coding styles
 - Separate coding of combinational logics and flip-flops



```
reg    [0:LEN-1] out;  
reg    [0:LEN-1] out_temp;
```

// Logic circuits

```
always @(in1 or in2 or ...)
```

```
out_temp <= combinational_circuits_codes;
```

// Flip-flops

```
always@(posedge clk or nedge reset) begin
```

```
if(~reset)
```

```
out <= 0;
```

```
else
```

```
out <= out_temp;
```

```
end
```

```
reg    [0:LEN-1] out;  
wire   [0:LEN-1] out_temp;
```

// Logic circuits

```
assign out_temp = combinational_circuits_codes;
```

// Flip-flops

```
always@(posedge clk or nedge reset) begin
```

```
if(~reset)
```

```
out <= 0;
```

```
else
```

```
out <= out_temp;
```


```
end
```




Finite State Machine

- Moore Machine

 - Output y depends on the current state, not input x .
- Output y is synchronized with the state s .



Current State	Next State		output y
	Input $x=0$	Input $x=1$	
s_0	s_2	s_1	0
s_1	s_0	s_2	0
s_2	s_1	s_0	1



Moore Machine

- Moore Machine Coding Style

```
module moore(reset, clk, x, y);  
input reset, clk, x;  
output y;  
reg y;  
parameter s0=2'b00, s1=2'b01, s2=2'b10;  
reg [0:1] ps, ns;
```

```
always@(reset or ps)  
begin  
    if (reset)  
        begin  
            ns = s0; y = 0;  
        end  
    else  
        begin  
            case(ps)
```

```
    s0: begin  
        if (x == 0)  
            ns = s2;  
        else ns = s1;  
        y = 0;  
    end
```

```
    s1: begin  
        if (x == 0)  
            ns = s0;  
        else ns = s2;  
        y = 0;  
    end
```

```
    .....  
endcase  
end end // else & always
```


```
always@(posedge clk or negedge reset)  
if (~reset)  
    ps<= s0;  
else  
    ps<= ns;  
endmodule
```



Finite State Machine

- Mealy Machine

 - Output y depends on both the current state and input x .
- Output y is synchronized with the input x .



Current State	Next State		Output y	
	Input $x=0$	Input $x=1$	Input $x=0$	Input $x=1$
s_0	s_2	s_1	0	0
s_1	s_0	s_2	0	0
s_2	s_1	s_0	1	1



Mealy Machine

- Mealy Machine Coding Style

```
module mealy(reset, clk, x, y);
input reset, clk, x;
output y;
reg y;
parameter s0=2'b00, s1=2'b01, s2=2'b10;
reg [0:1] ps, ns;
always@(reset or ps)
begin
    if (reset)
        begin
            ns = s0; y = 0;
        end
    else
        begin
```

```
        case(ps)
            s0: begin
                if (x == 0)
                    ns = s2;
                else ns = s1;
                if (x == 0)
                    y = 0;
                else y = 0;
            end
            s1: begin
                .....
            endcase
        end end // else & always

always@(posedge clk or negedge reset)
    if (~reset)
        ps<= s0;
    else
        ps<= ns;
endmodule
```

Outline

- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits



Behavior Modeling





- In behavior modeling, you must specify your circuit's
 - Action
 - How to model the circuit's behavior
 - Timing control
 - Timing
 - Condition
- Verilog supports the following structures for behavior modeling
 - Procedural block
 - Procedural assignment
 - Timing control
 - Control statement



Procedural Blocks

  - In Verilog, procedural blocks are basis of behavior modeling
- Procedural blocks are of two types
 - initial procedural block, which executes only once
 - always procedural block, which executes in a loop






Procedural Blocks

- All procedural blocks are activated at simulation time 0.
 - The block will not be executed until the enabling condition evaluates TRUE.
 - Without the enabling condition, the block will be executed immediately.


Activated at simulation time 0

 

Statement will not be executed until the condition *c* is TRUE.



Procedural Blocks

 

```
• module clock_gen(phi1,phi2);  
• output phi1,phi2;  
• reg phi1,phi2;
```

```
• initial  
• begin  
• phi1=0;phi2=0  
• end
```

```
• always  
• #100 phi1=~phi1;
```

```
• always @(posedge phi1)  
• begin  
• phi2=1;  
• #50 phi2=0;  
• #50 phi2=1;  
• #50 phi2=0;  
• end  
• endmodule
```

This procedural block is activated and executed at simulation time 0

This procedural block is activated at simulation time 0 and is always executed

This procedural block is activated at simulation time 0 but executed at positive edge of phi1



Procedural Blocks

- Three components
 - Procedural assignment statements
 - High-level programming language constructs
 - Timing controls
- Using the first two components to model the actions of the circuit.
- Using **timing controls** to model when should these actions happen.

Procedural Timing Control



- Three types
 - Simple delay control
 - `#50 clk=~clk;`
 - Event control
 - `@(a or b or ci) sum=a+b+ci;`
 - `@(posedge clk) q=d;`
 - Level-sensitive timing control



Block Statements

- Group two or more statements together
 - Sequential blocks
 - Enclosed by keyword **begin** and **end**
 - Parallel blocks
 - Enclosed by keyword **fork** and **join**

```
begin
    #10 out='d10;
    #10 out='d43;
    #10 out='d25;
    #10 out='d86;
end
```

Equivalent

```
fork
    #10 out='d10;
    #20 out='d43;
    #30 out='d25;
    #40 out='d86;
join
```



Blocking and Non-blocking Assignments

- Procedural assignments update the value of register under the control of the procedure flow constructs.
- Blocking procedure assignment
Basic form : $\langle \text{lvalue} \rangle = \langle \text{timing_control} \rangle \langle \text{expression} \rangle$
- Non-Blocking procedure assignment
Basic form : $\langle \text{lvalue} \rangle \leq \langle \text{timing_control} \rangle \langle \text{expression} \rangle$

```
initial begin
  a=0;
  b=1;
  c=0;
end
always c = #5 ~c;
```

```
always @(posedge c)
begin
  a=b; // 1
  b=a; // 1
end
```

Blocking

```
always @(posedge c)
begin
  a<=b; // 1
  b<=a; // 0
end
```

Non-Blocking




Blocking and Non-blocking Assignments

- Blocking assignments
 - Evaluate the RHS expression and **stores** the value in the LHS register immediately

```
initial begin
  a = #10 1;
  $display("current time = %t a = %b", $time, a);
end
```

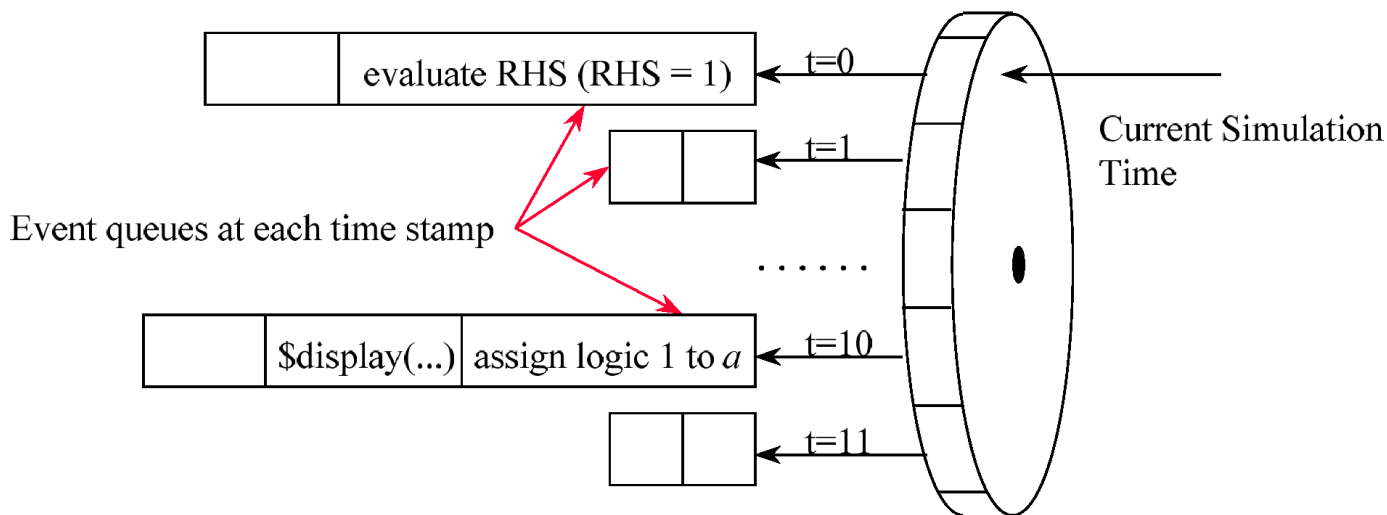simulation
result → current time = 10, a = 1





Blocking and Non-blocking Assignments

- Non-blocking assignments
 - It evaluate the RHS expression and **schedules** to update the value in the LHS register
 - It updates the LHS only after evaluating all the RHS

initial begin


```
a <= #10 1;
```

```
$display("current time = %t a = %b", $time, a);
```

```
end
```

simulation
result

current time = 0, a = x

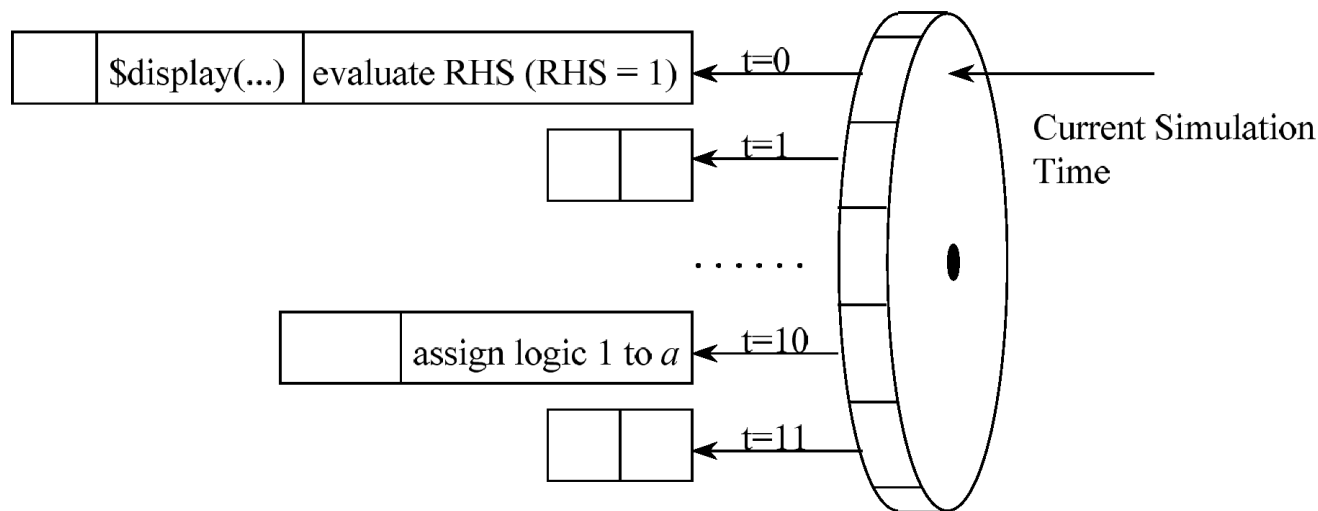


Blocking and Non-blocking Assignments




Bad: Circuit from blocking assignment.
 
```
always @(posedge clk)
begin
    b=a;
    a=b;
end
```



Good: Circuit from nonblocking assignment.
 
```
always @(posedge clk)
begin
    b<=a;
    a<=b;
end
```



Outline




- Verilog Coding for Sequential Logics
- Behavior Modeling
- Examples of Sequential Circuits



D-type Flip Flop
 
```
module dff(  
    q, // output  
    d, // input  
    clk, // global clock  
    rst_n // active low reset  
);  
  
output q; // output  
input d; // input  
input clk; // global clock  
input rst_n; // active low reset  
  
reg q; // output (in always block)  
  
always @(posedge clk or negedge  
rst_n)  
    if (~rst_n)  
        q<=0;  
    else  
        q<=d;  
  
endmodule
```



Binary Up Counter



```
`define BCD_BIT_WIDTH 4
`define BCD_ZERO 4'd0
`define BCD_ONE 4'd1
`define BCD_NINE 4'd9
module bcdcounter(
    q, // output
    clk, // global clock
    rst_n // active low reset
);


output [`BCD_BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [`BCD_BIT_WIDTH-1:0] q; // output (in always block)
reg [`BCD_BIT_WIDTH-1:0] q_tmp; // input to dff (in always block)

// Combinational logics
always @(q)
    q_tmp = q + `BCD_ONE;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
    if (~rst_n) q<=`BCD_BIT_WIDTH'd0;
    else q<=q_tmp;

endmodule
```

 

Frequency Divider



```
`define FREQ_DIV_BIT 24
module freq_div(
  clk_out, // divided clock output
  clk, // global clock input
  rst_n // active low reset
);


output clk_out; // divided output
input clk; // global clock input
input rst_n; // active low reset

reg clk_out; // clk output (in always block)
reg [`FREQ_DIV_BIT-2:0] cnt; // remainder of the counter
reg [`FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

// Combinational logics: increment, neglecting overflow
always @(clk_out or cnt)
  cnt_tmp = {clk_out,cnt} + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n) {clk_out, cnt}<=`FREQ_DIV_BIT'd0;
  else {clk_out,cnt}<=cnt_tmp;

endmodule
```

 

cnt_tmp[23:0]



cnt[22:0]



Modularized Shift Register Design



Shift Register

  

shifter.v




```
`define BIT_WIDTH 4
module shifter(
    q, // shifter output
    clk, // global clock
    rst_n // active low reset
);

output [`BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [`BIT_WIDTH-1:0] q; // output

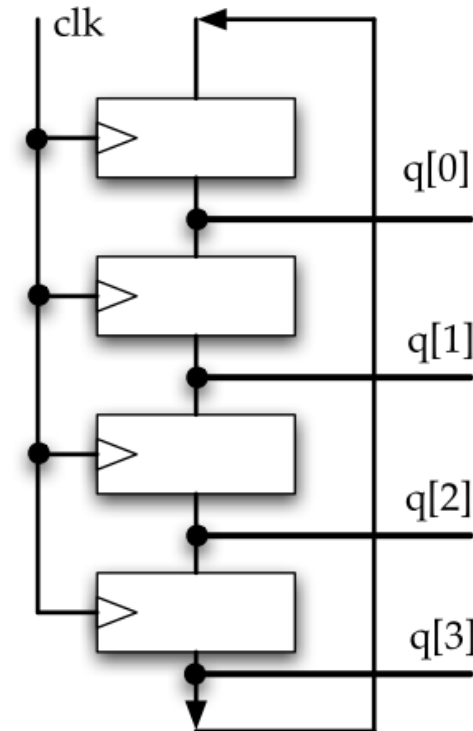// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
    if (~rst_n)
        begin
            q<=`BIT_WIDTH'b0101;
        end
    else
        begin
            q[0]<=q[3];
            q[1]<=q[0];
            q[2]<=q[1];
            q[3]<=q[2];
        end
    end
endmodule
```



Initial value $q = 0101$

shiftreg.v



```
`define BIT_WIDTH 4
module shift_reg(
    q, // LED output
    clk, // global clock
    rst_n // active low reset
);

output [ `BIT_WIDTH-1:0] q; // LED output
input clk; // global clock
input rst_n; // active low reset

wire clk_d; // divided clock
wire [ `BIT_WIDTH-1:0] q; // LED output
```

```
// Insert frequency divider (freq_div.v)
freq_div U_FD(
    .clk_out(clk_d), // divided clock output
    .clk(clk), // clock from the crystal
    .rst_n(rst_n) // active low reset
);

// Insert shifter (shifter.v)
shifter U_D(
    .q(q), // shifter output
    .clk(clk_d), // clock from the frequency divider
    .rst_n(rst_n) // active low reset
);

endmodule
```