

Lab 2 - FPGA Emulation Report

106033233 資工大四 周聖諺

Lab 2 - 1: 4-Bit Binary-To-Gray-Code Converter

Design Specification

Source Code

Input: a, b, c, d

Output: w, x, y, z

Design Implementation

First, we can observe that the MSB of the Gray code and binary code are always the same so it doesn't need any conversion. The Boolean equation is $a = w$

In addition, if you list the table of the conversion from 4-bit Gray-code to binary code, you can observe that $a \oplus b = x$, $b \oplus c = y$ and, $c \oplus d = z$. Thus, we can design the circuit as the following code.

Boolean Equation:

$$a = w$$

$$a \oplus b = x$$

$$b \oplus c = y$$

$$c \oplus d = z$$

BCD to Gray Code Truth Table

Decimal	Binary Code (abcd)	Gray Code (wxyz)
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1100
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

Verilog Code


```
assign w = a;  
assign x = a ^ b;  
assign y = b ^ c;  
assign z = c ^ d;
```

I/O Pin Assignment

I/O	a	b	c	d	w	x	y	z
LOC	W17	W16	V16	V17	V19	U19	E19	U16


Block Diagram

1.2

 

2

RTL Simulation

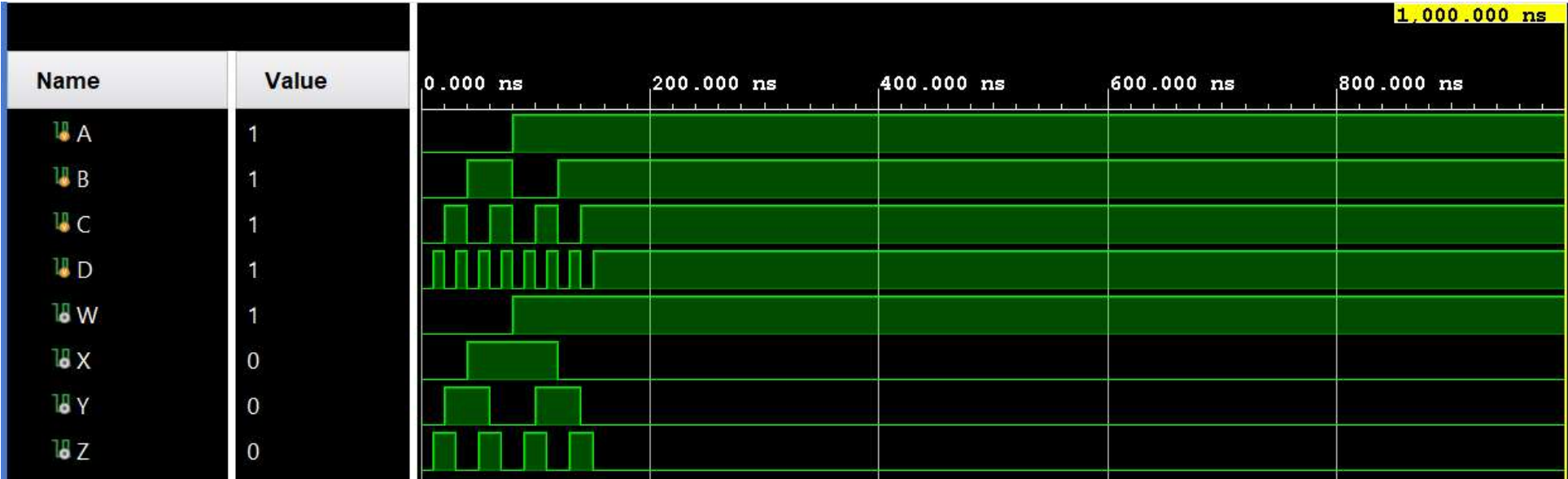

Lab 2 - 2: Binary to 7-Segment Display Decoder

[Source Code](#)

Design Specification

Binary to 7-Segment Display Decoder

Input [3:0]i

Output [3:0]d, [3:0]P, [7:0]D

Design Implementation

4-Bits Binary Displayer

It's quite easy to display the 4-bit binary number. All we need to do is to light the LED up while the corresponding bit is 1, vice versa.

Boolean Equation:

$$\begin{aligned}d[0] &= i[0] \\d[1] &= i[1] \\d[2] &= i[2] \\d[3] &= i[3]\end{aligned}$$

Verilog Code

```
assign d = i;
```

7-Segment Display Decoder

We design the logic circuit with K-map to implement the decoder, but in Verilog, to simplify the code, we implement the logic with switch-case.

Boolean Equation:

$$\begin{aligned}D[0] = & [i[0] \wedge (\neg i[1]) \wedge (\neg(i[3] \oplus i[2])) \\& \vee [(\neg i[1]) \wedge (\neg i[0]) \wedge (\neg i[3]) \wedge i[2]] \\& \vee [i[1] \wedge i[0] \wedge i[3] \wedge (\neg i[2])]]\end{aligned}$$

$$\begin{aligned}D[1] = & [(\neg i[3]) \wedge i[2] \wedge (i[1] \oplus i[0])] \\& \vee [i[3] \wedge i[2] \wedge (i[1] \vee ((\neg i[1]) \wedge (\neg i[0])))] \\& \vee [i[3] \wedge i[1] \wedge i[0]]\end{aligned}$$

$$\begin{aligned}D[2] = & [i[3] \wedge i[2] \wedge (i[1] \vee (\neg i[0]))] \\& \vee [(\neg i[3]) \wedge (\neg i[2]) \wedge i[1] \wedge (\neg i[0])]\end{aligned}$$

$$\begin{aligned}D[3] = & [(\neg i[1]) \wedge i[0] \wedge (\neg i[3]) \wedge (\neg i[2])] \\& \vee [i[1] \wedge i[0] \wedge i[2]] \\& \vee [(\neg(i[1] \oplus i[0])) \wedge ((\neg i[3]) \wedge i[2])] \\& \vee [i[1] \wedge (\neg i[0]) \wedge i[3] \wedge (\neg i[2])]\end{aligned}$$

$$D[4] = [(\neg i[1]) \wedge i[0] \wedge ((\neg i[3]) \vee (i[3] \wedge (\neg i[2])))] \\ \vee [i[1] \wedge i[0] \wedge (\neg i[3])] \\ \vee [((\neg i[1]) \vee i[0]) \wedge (\neg i[3]) \wedge i[2]]$$

$$D[5] = [(i[1] \vee i[0]) \wedge (\neg i[3]) \wedge (\neg i[2])] \\ \vee [i[1] \wedge i[0] \wedge (\neg i[3])] \\ \vee [i[1] \wedge (\neg i[0]) \wedge (\neg (i[3] \oplus i[2]))]$$


$$D[6] = [(\neg i[1]) \wedge (\neg i[3]) \wedge (\neg i[2])] \\ \vee [(\neg i[1]) \wedge (\neg i[0]) \wedge (\neg (i[3] \oplus i[2]))] \\ \vee [i[1] \wedge i[0] \wedge (\neg i[3]) \wedge i[2]]$$

$$D[7] = 1$$


Verilog Code

```
assign P = ~4'b0001;
always@(i)
  case(i)
    4'd0: D=8'b0000001_1;
    4'd1: D=8'b1001111_1;
    4'd2: D=8'b0010010_1;
    4'd3: D=8'b0000110_1;
    4'd4: D=8'b1001100_1;
    4'd5: D=8'b0100100_1;
    4'd6: D=8'b0100000_1;
    4'd7: D=8'b0001111_1;
    4'd8: D=8'b0000000_1;
    4'd9: D=8'b0000100_1;
    4'd10: D=8'b0001000_1;
    4'd11: D=8'b1100000_1;
    4'd12: D=8'b0110001_1;
    4'd13: D=8'b1000010_1;
    4'd14: D=8'b0110000_1;
    4'd15: D=8'b0111000_1;
    default: D= 8'b0111000_1;
  endcase
```


Lab2 - 2 Binary to 7-Segment Display

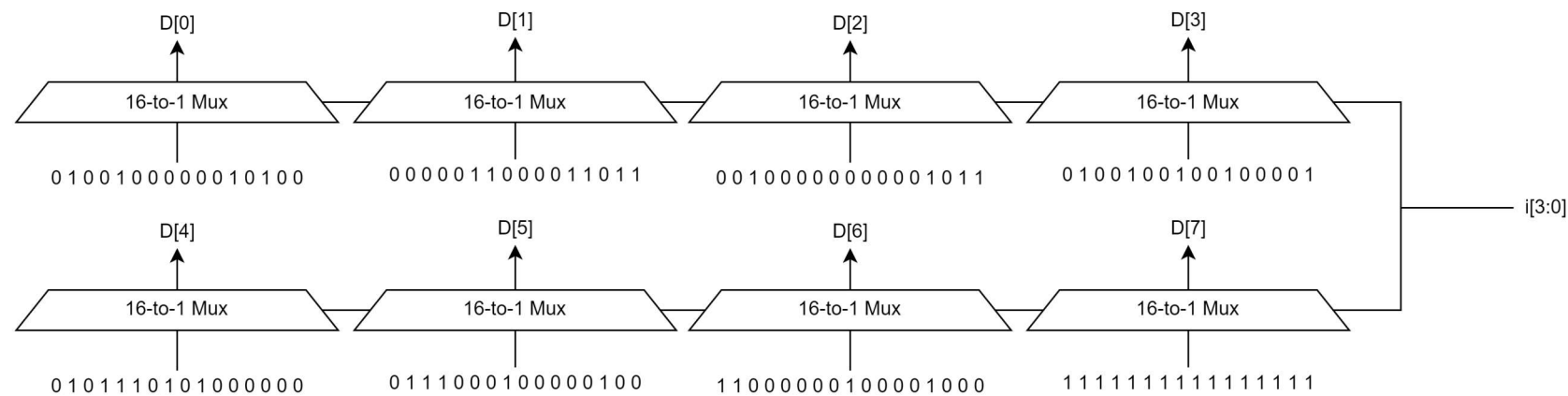

16-to-1 Mux

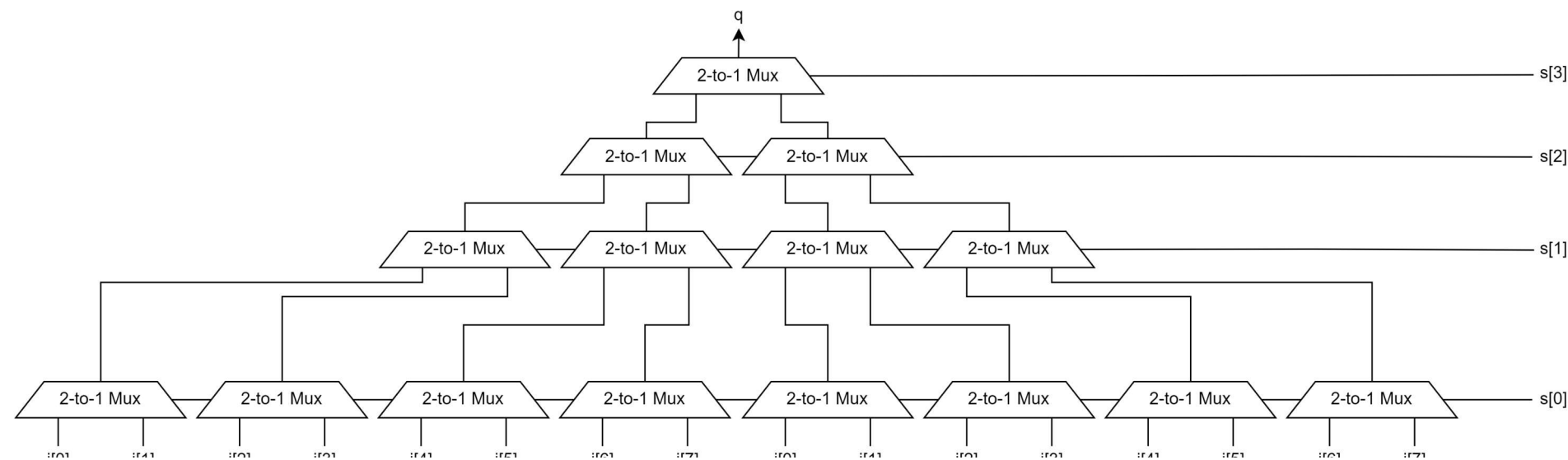

2-to-1 Mux

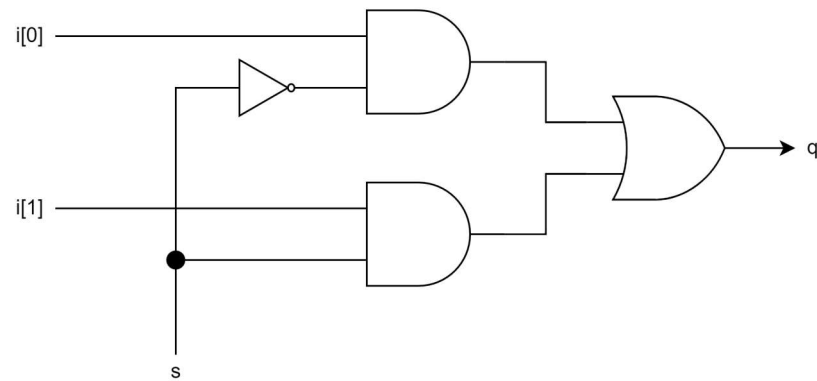

RTL Simulation



I/O Pin Assignment

I/O	i[3]	i[2]	i[1]	i[0]	d[3]	d[2]	d[1]	d[0]
LOC	W17	W16	V16	V17	V19	U19	E19	U16

I/O	P[3]	P[2]	P[1]	P[0]	D[7]	D[6]	D[5]	D[4]	D[3]	D[2]	D[1]	D[0]
LOC	W4	V4	U4	U2	W7	W6	U8	V8	U5	V5	U7	V7

Lab 2 - 3: Bull-And-Cow Game

Design Specification

[Source Code](#)

Bull-And-Cow Game

Input [3:0]A_D1, [3:0]A_D2, [3:0]B_D1, [3:0]B_D2,

Output [2:0] bull, [2:0] cow

Design Implementation

Bull-And-Cow Game

In the file *lab2_3.v*, I implement the logic circuit of the Bull-And-Cow game. The Bull shows the number of the right numbers in the right positions, which means the digit 1 of guessed number is the same as the digit of the correct number, so as digit 2. Denote the variable A_D1 and A_D2 are the first digit and the second digit of guessed number and B_D1 and B_D2 are the digits of the correct number. If A_D1 is equal to B_D1 and A_D2 is equal to B_D2, there are 2 bulls. If only one digit is in the right place, there is 1 bull, which can be implemented with XOR gate.

The number of cows represents the correct digits in the wrong place. As a result, If A_D1 is equal to B_D2 and A_D2 is equal to B_D1, there will be 2 cows.

Following are the Boolean equation and the code.

Boolean Equation

$$2 \text{ bull} = ((A_{D1}[0] \odot B_{D1}[0]) \wedge (A_{D1}[1] \odot B_{D1}[1]) \wedge (A_{D1}[2] \odot B_{D1}[2]) \wedge (A_{D1}[3] \odot B_{D1}[3])) \wedge ((A_{D2}[0] \odot B_{D2}[0]) \wedge (A_{D2}[1] \odot B_{D2}[1]) \wedge (A_{D2}[2] \odot B_{D2}[2]) \wedge (A_{D2}[3] \odot B_{D2}[3]))$$

$$1 \text{ bull} = ((A_{D1}[0] \odot B_{D1}[0]) \wedge (A_{D1}[1] \odot B_{D1}[1]) \wedge (A_{D1}[2] \odot B_{D1}[2]) \wedge (A_{D1}[3] \odot B_{D1}[3])) \oplus ((A_{D2}[0] \odot B_{D2}[0]) \wedge (A_{D2}[1] \odot B_{D2}[1]) \wedge (A_{D2}[2] \odot B_{D2}[2]) \wedge (A_{D2}[3] \odot B_{D2}[3]))$$

$$0 \text{ bull} = \neg((A_{D1}[0] \odot B_{D1}[0]) \wedge (A_{D1}[1] \odot B_{D1}[1]) \wedge (A_{D1}[2] \odot B_{D1}[2]) \wedge (A_{D1}[3] \odot B_{D1}[3])) \wedge \neg((A_{D2}[0] \odot B_{D2}[0]) \wedge (A_{D2}[1] \odot B_{D2}[1]) \wedge (A_{D2}[2] \odot B_{D2}[2]) \wedge (A_{D2}[3] \odot B_{D2}[3]))$$

$$2 \text{ cow} = ((A_{D1}[0] \odot B_{D2}[0]) \wedge (A_{D1}[1] \odot B_{D2}[1]) \wedge (A_{D1}[2] \odot B_{D2}[2]) \wedge (A_{D1}[3] \odot B_{D2}[3])) \wedge ((A_{D2}[0] \odot B_{D1}[0]) \wedge (A_{D2}[1] \odot B_{D1}[1]) \wedge (A_{D2}[2] \odot B_{D1}[2]) \wedge (A_{D2}[3] \odot B_{D1}[3]))$$

$$1 \text{ cow} = ((A_{D1}[0] \odot B_{D2}[0]) \wedge (A_{D1}[1] \odot B_{D2}[1]) \wedge (A_{D1}[2] \odot B_{D2}[2]) \wedge (A_{D1}[3] \odot B_{D2}[3])) \oplus ((A_{D2}[0] \odot B_{D1}[0]) \wedge (A_{D2}[1] \odot B_{D1}[1]) \wedge (A_{D2}[2] \odot B_{D1}[2]) \wedge (A_{D2}[3] \odot B_{D1}[3]))$$

$$0 \text{ cow} = \neg((A_{D1}[0] \odot B_{D2}[0]) \wedge (A_{D1}[1] \odot B_{D2}[1]) \wedge (A_{D1}[2] \odot B_{D2}[2]) \wedge (A_{D1}[3] \odot B_{D2}[3])) \wedge \neg((A_{D2}[0] \odot B_{D1}[0]) \wedge (A_{D2}[1] \odot B_{D1}[1]) \wedge (A_{D2}[2] \odot B_{D1}[2]) \wedge (A_{D2}[3] \odot B_{D1}[3]))$$

where \odot denote the XNOR gate(Not Exclusive OR)

Verilog Code

```
reg [2:0]BULL;
reg [2:0]COW;

assign bull[2] = (A_D1 == B_D1) && (A_D2 == B_D2);
assign bull[1] = (A_D1 == B_D1) ^ (A_D2 == B_D2);
assign bull[0] = (~(A_D1 == B_D1) && ~(A_D2 == B_D2));
```





```





assign cow[2] = (A_D1 == B_D2) && (A_D2 == B_D1);
assign cow[1] = (A_D1 == B_D2) ^ (A_D2 == B_D1);
assign cow[0] = (!(A_D1 == B_D2) && ~(A_D2 == B_D1));

```


Logic Diagram

Lab2 - 3 Bull and Cow Game

    

 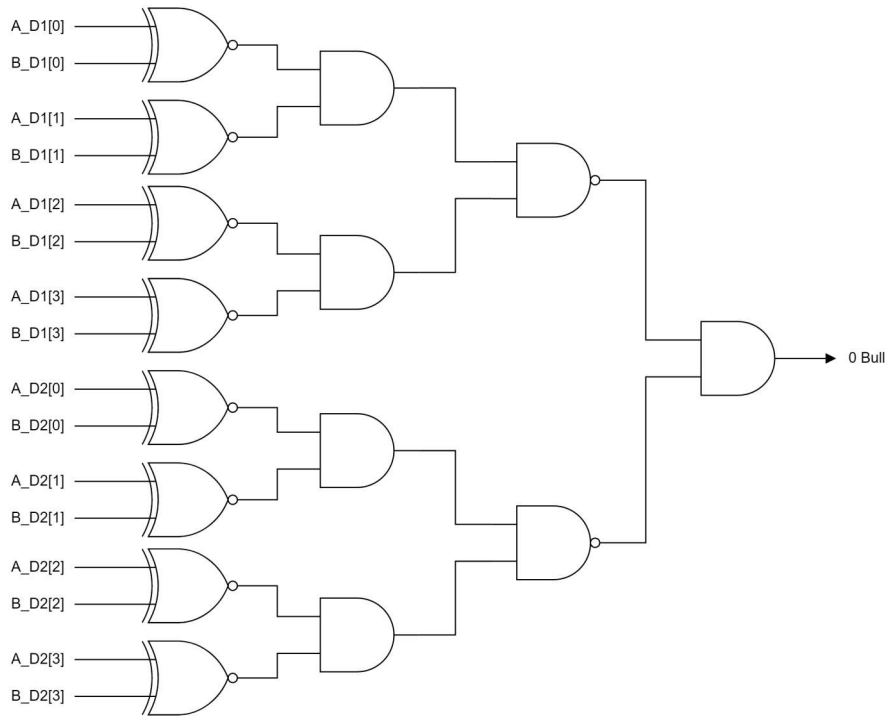 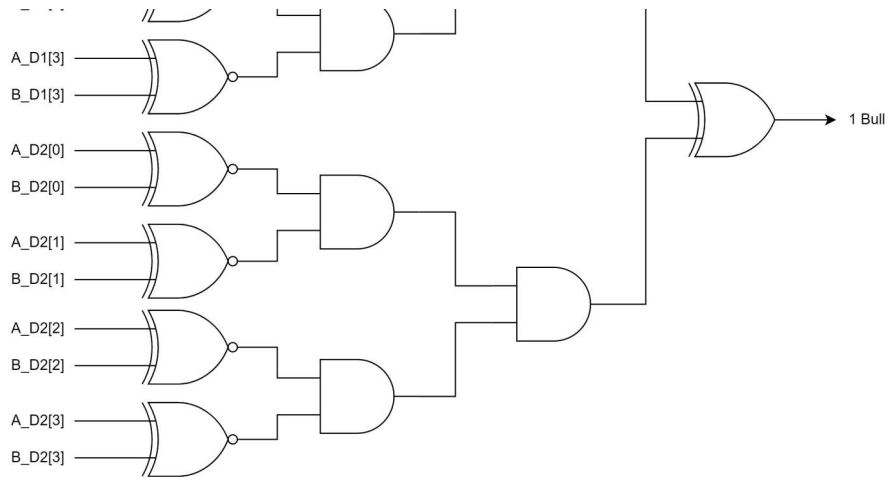

RTL Simulation

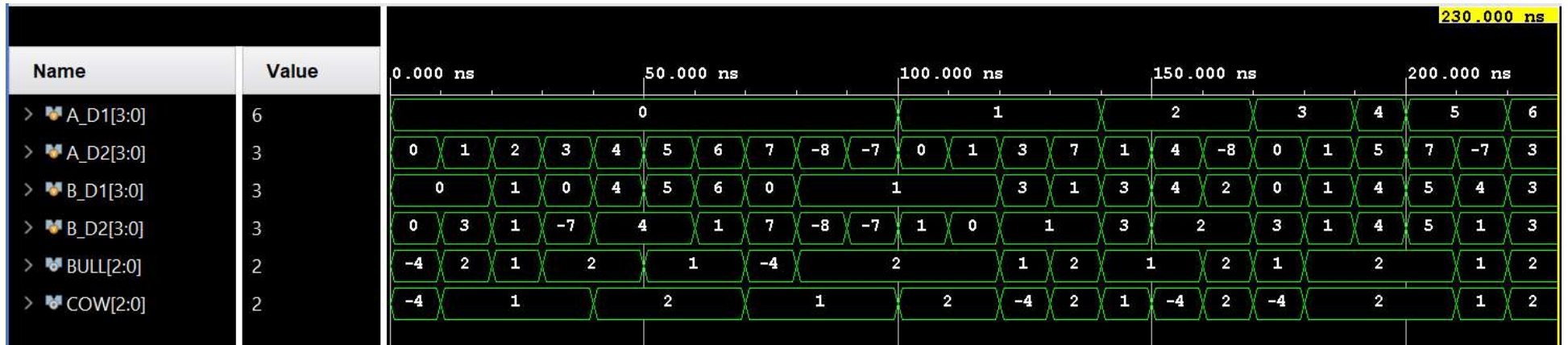

I/O Pin Assignment

I/O	A_D1[0]	A_D1[1]	A_D1[2]	A_D1[3]	A_D2[0]	A_D2[1]	A_D2[2]	A_D2[3]
LOC	V17	V16	W16	W17	W15	V15	W14	W13

I/O	A_D1[0]	A_D1[1]	A_D1[2]	A_D1[3]	A_D2[0]	A_D2[1]	A_D2[2]	A_D2[3]
LOC	V17	V16	W16	W17	W15	V15	W14	W13

I/O	bull[2]	bull[1]	bull[0]	cow[2]	cow[1]	cow[0]
LOC	U19	E19	U16	U15	W18	V19

Discussion

In the lab 1-3, we've learned how to implement a combinatorial circuit on the FPGA board, how to set up the ports and how to synthesis and generate the bit-stream. Note that the 7-segment display is low-activate.

Conclusion

In this lab, I've learned that how to design a logical circuit with Verilog and simulate the behavior with RTL simulation. In addition, I've also learned how to program the FPGA and run the designed circuit on it.

Reference

- [Java T Point - Binary to Gray code conversion](#)

Provide the design example of the binary-to-Gray-code convertor.