

Lab 5 - Timer and Stopwatch

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

2022-03-28

Contents

Lab 5 - Timer and Stopwatch Report	4
Lab 5 - Pre Lab: 40-Second Timer	4
Design Specification	4
Design Implementation	5
Global Variables	5
Debounce	6
One-Pulse	6
Finite State Machine	7
Frequency Divider	8
2-Digit Synchronous Binary Down Counter	9
LEDs Controller	11
Extractor	11
Binary To 7-Segment Convertor	12
7-Segment Display	13
40-Second Timer	15
I/O Pin Assignment	16
Block Diagram	17
RTL Simulation	18
Lab 5-1: 40-Second Down Counter	18
Lab 5 - 2: Stopwatch	18
Design Specification	18
Design Implementation	20
Global Variables	20
Debounce	20
One-Pulse	20
Finite State Machine	22
Lap Controller	23
Frequency Divider	24
2-Digit Synchronous Binary Up Counter	24
LEDs Controller	25
Minute-Second Separator	26
Binary To 7-Segment Convertor	27
7-Segment Display	27
7-Segment Time Display	27
Stopwatch	28
I/O Pin Assignment	29

Block Diagram	31
RTL Simulation	32
Lab 5 - 3: Timer	32
Design Specification	32
Design Implementation	33
Global Variables	33
Debounce	34
One-Pulse	34
Finite State Machine	34
Frequency Divider	37
2-Digit Synchronous Binary Down Counter	37
LEDs Controller	37
Minute-Second Separator	38
Binary To 7-Segment Convertor	38
7-Segment Display	38
7-Segment Time Display	38
Timer	38
I/O Pin Assignment	40
Block Diagram	41
RTL Simulation	41
Discussion	42
Conclusion	42
Reference	42

Lab 5 - Timer and Stopwatch Report

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

Lab 5 - Pre Lab: 40-Second Timer

Design Specification

Source Code

Debounce

Input: rst, clk, push

Output: push_debounced

One-Pulse

Input: rst, clk, push

Output: push_onepulse

Finite State Machine

Input pause, clk, restart

Output is_pause, is_restart

Frequency Divider

Input: rst, clk

Output: clk_out

2-Digit Synchronous Binary Down Counter

Input: rst, clk

Output [7:0]q

LEDs Controller

Input: q, is_pause, is_restart

Output: leds

Extractor

Input: [7:0] x

Output: [3:0] d1, [3:0] d2

Binary To 7-Segment Convertor

Input: [3:0] i

Output: [3:0] P, [7:0] D

7-Segment7 Frequency Divider

Input: clk, rst

Output: clk_out

7-Segment Display

Output: [0:3] d_sel, [7:0] d_out

Input: clk, rst, [7:0] d0, [7:0] d1, [7:0] d2, [7:0] d3

40-Second Timer

Output [15:0] leds, [3:0] D_SEL, [7:0] D_OUT

Input restart, push, rst, clk

Design Implementation

Global Variables The global variables are used across the whole project.

```

1 // Segment-7 Displayer
2 `define SEGMENT_7_INPUT_BITS_N 4
3 `define SEGMENT_7_DISPALY_DIGIT_N 4
4 `define SEGMENT_7_SEGMENT_N 8
5 `define SEGMENT_7_NONE `SEGMENT_7_SEGMENT_N'b1111111_1
6 `define SEGMENT_7_EMPTY `SEGMENT_7_SEGMENT_N'b1111111_0
7
8 // Segment-7 Displayer Frequency Divider
9 `define SEGMENT_7_FREQ_DIV_BITS 30
10 // 1000 Hz
11 `define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000
12 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd2
13 // 1 Hz
14 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd5000000
15 `define RST_OFF 1'b1
16
17 // BCD Counter
18 `define BCD_COUNTER_BITS 8
19 `define BCD_COUNTER_LIMIT `BCD_COUNTER_BITS'd40
20 `define BCD_COUNTER_ZERO `BCD_COUNTER_BITS'd0

```

```

21
22 // Frequency Divider
23 `define FREQ_DIV_BITS 30
24 // 1 Hz
25 `define FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000000
26
27 // LED control
28 `define LEDS_NUM 16

```

Debounce For each click, the module will delay 4 clock cycle and then raise the debounce pulse. I use 4 registers to represent the delay state and send a pulse while 4 registers are all 1s.

```

1 module debounce (
2     rst,
3     clk,
4     push,
5     push_debounced
6 );
7
8 input rst;
9 input clk;
10 input push;
11 output push_debounced;
12 // declare the outputs
13 reg push_debounced;
14 // declare the shifting registers
15 reg[3:0] push_window;
16
17 always @(posedge clk or posedge rst)
18 begin
19     if (~rst) begin
20         push_window <= 4'b0;
21         push_debounced <= 1'b0;
22     end else begin
23         push_window <= {push, push_window[3:1]};
24
25         if (push_window[3:0] == 4'b1111) begin
26             push_debounced <= 1'b1;
27         end else begin
28             push_debounced <= 1'b0;
29         end
30     end
31 end
32 endmodule

```

One-Pulse The one-pulse module raise a pulse while the debounce module raises a pulse. As a result, it will produce high voltage while the previous debounce signal is higher than the current de-

bounce signal.

```
1 module onepulse (  
2     rst,  
3     clk,  
4     push,  
5     push_onepulse  
6 );  
7  
8 input clk, rst;  
9 input push;  
10 output push_onepulse;  
11 // internal registers  
12 reg push_onepulse_next;  
13 reg push_debounced_delay;  
14 reg push_onepulse;  
15 wire push_debounced;  
16  
17 debounce U0(.clk(clk), .rst(rst), .push(push), .push_debounced(  
18     push_debounced));  
19  
20 always @* begin  
21     push_onepulse_next = push_debounced & ~push_debounced_delay;  
22 end  
23  
24 always @(posedge clk or posedge rst)  
25 begin  
26     if (~rst) begin  
27         push_onepulse <= 1'b0;  
28         push_debounced_delay <= 1'b0;  
29     end else begin  
30         push_onepulse <= push_onepulse_next;  
31         push_debounced_delay <= push_debounced;  
32     end  
33 end  
34 endmodule
```

Finite State Machine The finite state machine controls 2 signals: `is_pause` and `is_restart`. The down counter will pause while the signal `is_pause` is at high voltage and resume to count while the signal is at low voltage. It is controlled independently, so I only need to inverse the signal whenever the button `restart` is pressed.

On the other hand, the down counter will reset to 0 when the signal `is_restart` raises. It only depends on `restart` button, so we only need to inverse the signal whenever the button is clicked.

```
1 `define STATE_START 0  
2  
3 module fsm(  
4     is_pause,
```

```
5     is_restart,  
6     pause,  
7     clk,  
8     restart  
9 );  
10  
11     output is_pause;  
12     output is_restart;  
13     input pause;  
14     input clk;  
15     input restart;  
16  
17     reg is_restart;  
18     reg is_pause;  
19     reg state;  
20  
21     initial  
22     begin  
23         state = `STATE_START;  
24     end  
25  
26     always@(posedge restart)  
27     begin  
28         is_restart = is_restart ^ 1;  
29     end  
30  
31     always@(posedge pause)  
32     begin  
33         if(state == `STATE_PAUSE)  
34             begin  
35                 state = `STATE_START;  
36                 is_pause = 0;  
37             end  
38         else if(state == `STATE_START)  
39             begin  
40                 state = `STATE_PAUSE;  
41                 is_pause = 1;  
42             end  
43     end  
44 endmodule
```

Frequency Divider To generate the 1 Hz clock, I use variables counter_in and counter_out to count from 0 to 50M. The counter_in will store the value for the next time step and pass the value to the counter_out when the clock raises. The reason why we need 50M counting is each counting is triggered only when the clock raises, so the circuit will count 1 more for every twice clock pulses.

```
1  `include "global.v"  
2  
3  //`define FREQ_DIV_BITS 30
```



```
4 //`define FREQ_DIV_COUNT `FREQ_DIV_BITS'd1000000
5 //`define FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000000
6
7 module frequency_divider(
8     clk_out,
9     clk,
10    rst
11 );
12
13 input clk;
14 input rst;
15 output clk_out;
16
17 reg clk_in;
18 reg clk_out;
19 reg [`FREQ_DIV_BITS-1:0] counter_in;
20 reg [`FREQ_DIV_BITS-1:0] counter_out;
21
22 always@(counter_out or clk_out)
23     if(counter_out < (`FREQ_DIV_COUNT - 1))
24         begin
25             counter_in <= counter_out + `FREQ_DIV_BITS'd1;
26             clk_in <= clk_out;
27         end
28     else
29         begin
30             counter_in <= `FREQ_DIV_BITS'd0;
31             clk_in <= ~clk_out;
32         end
33
34 always@(posedge clk or negedge rst)
35     if(~rst)
36         begin
37             counter_out <= `FREQ_DIV_BITS'd0;
38             clk_out <= 1'd0;
39         end
40     else
41         begin
42             counter_out <= counter_in;
43             clk_out <= clk_in;
44         end
45 endmodule
```

2-Digit Synchronous Binary Down Counter To implement the binary down counter, I use a variable `q_in` to count from 0 to 15. Whenever the output of the counter `q` changes, the variable `q_in` should be changed to `q - 1`. In addition, when the circuit detects the raise of the clock, the output of the counter will change to the variable `q_in`. On the other hand, if the reset switch to 0 or the counter hits 0, `q` will be reset to the upper limit 15.

Verilog Code

```
1  `include "global.v"
2
3  module binary_down_2digit_counter(
4      q,
5      clk,
6      rst,
7      is_pause
8  );
9
10     output [`BCD_COUNTER_BITS-1:0]q;
11     input  clk;
12     input  rst;
13     input  is_pause;
14
15     reg [`BCD_COUNTER_BITS-1:0]q;
16     reg [`BCD_COUNTER_BITS-1:0]q_in;
17
18     initial
19     begin
20         q <= `BCD_COUNTER_LIMIT;
21     end
22
23     always@(q)
24     begin
25         // if(q == (`BCD_COUNTER_LIMIT - `BCD_COUNTER_BITS'd1))
26         if(q <= `BCD_COUNTER_BITS'd1)
27             begin
28                 q_in <= `BCD_COUNTER_ZERO;
29             end
30         else
31             begin
32                 if(~is_pause)
33                     begin
34                         q_in <= q - `BCD_COUNTER_BITS'd1;
35                     end
36                 else
37                     begin
38                         q_in <= q;
39                     end
40             end
41         end
42
43     always@(posedge clk or negedge rst)
44     begin
45         if(~rst)
46             begin
47                 q <= `BCD_COUNTER_LIMIT;
48             end
49         else
```

```

50         begin
51             q <= q_in;
52         end
53     end
54 endmodule

```

LEDs Controller The LEDs will all light up whenever the the module counts to 0. In addition, `LED[0]` lights up when the counter is counting and goes out when the counter is paused.

```

1  `include "global.v"
2
3  module led_control(
4      q,
5      is_pause,
6      is_restart,
7      leds
8  );
9
10     input  [`BCD_COUNTER_BITS-1:0]q;
11     input  is_pause;
12     input  is_restart;
13     output [`LEDS_NUM-1:0]leds;
14
15     reg    [`LEDS_NUM-1:0]leds;
16
17     always@(q or is_pause or is_restart)
18     begin
19         if(q == `BCD_COUNTER_ZERO)
20             begin
21                 leds = `{LEDS_NUM{1'b1}};
22             end
23         else if((!is_pause) && (is_restart))
24             begin
25                 leds = `LEDS_NUM'b1;
26             end
27         else
28             begin
29                 leds = `LEDS_NUM'b0;
30             end
31     end
32 endmodule

```

Extractor I use mod of 10 to extract the first decimal digit and use divided by 10 to extract the second decimal digit.

```

1  `include "global.v"
2

```

```

3  module extract(
4      input  [`BCD_COUNTER_BITS-1:0] x,
5      output [`SEGMENT_7_INPUT_BITS_N-1:0] d1,
6      output [`SEGMENT_7_INPUT_BITS_N-1:0] d2
7  );
8
9      wire [`BCD_COUNTER_BITS-1:0] mod;
10     wire [`BCD_COUNTER_BITS-1:0] div;
11     assign mod = x % 10;
12     assign div = x / 10;
13
14     assign d1 = mod[`SEGMENT_7_INPUT_BITS_N-1:0];
15     assign d2 = div[`SEGMENT_7_INPUT_BITS_N-1:0];
16 endmodule

```

Binary To 7-Segment Convertor Convert 4-bit binary number to 7-segment display with switch-case syntax.

```

1  `include "global.v"
2
3  module segment7(
4      i,
5      P,
6      D
7  );
8
9      input  [`SEGMENT_7_INPUT_BITS_N:0] i;
10     output [`SEGMENT_7_DISPALY_DIGIT_N-1:0] P;
11     output [`SEGMENT_7_SEGMENT_N-1:0] D;
12
13     reg [`SEGMENT_7_SEGMENT_N-1:0] D;
14
15     assign P = ~4'b0001;
16     always@(i)
17         case(i)
18             `SEGMENT_7_INPUT_BITS_N'd0: D=`SEGMENT_7_SEGMENT_N'
19                 b0000001_1;
20             `SEGMENT_7_INPUT_BITS_N'd1: D=`SEGMENT_7_SEGMENT_N'
21                 b1001111_1;
22             `SEGMENT_7_INPUT_BITS_N'd2: D=`SEGMENT_7_SEGMENT_N'
23                 b0010010_1;
24             `SEGMENT_7_INPUT_BITS_N'd3: D=`SEGMENT_7_SEGMENT_N'
25                 b0000110_1;
26             `SEGMENT_7_INPUT_BITS_N'd4: D=`SEGMENT_7_SEGMENT_N'
27                 b1001100_1;
28             `SEGMENT_7_INPUT_BITS_N'd5: D=`SEGMENT_7_SEGMENT_N'
29                 b0100100_1;
30             `SEGMENT_7_INPUT_BITS_N'd6: D=`SEGMENT_7_SEGMENT_N'
31                 b0100000_1;

```

```

25         `SEGMENT_7_INPUT_BITS_N'd7: D=`SEGMENT_7_SEGMENT_N'
           b0001111_1;
26         `SEGMENT_7_INPUT_BITS_N'd8: D=`SEGMENT_7_SEGMENT_N'
           b0000000_1;
27         `SEGMENT_7_INPUT_BITS_N'd9: D=`SEGMENT_7_SEGMENT_N'
           b0000100_1;
28         `SEGMENT_7_INPUT_BITS_N'd10: D=`SEGMENT_7_SEGMENT_N'
           b0001000_1;
29         `SEGMENT_7_INPUT_BITS_N'd11: D=`SEGMENT_7_SEGMENT_N'
           b1100000_1;
30         `SEGMENT_7_INPUT_BITS_N'd12: D=`SEGMENT_7_SEGMENT_N'
           b0110001_1;
31         `SEGMENT_7_INPUT_BITS_N'd13: D=`SEGMENT_7_SEGMENT_N'
           b1000010_1;
32         `SEGMENT_7_INPUT_BITS_N'd14: D=`SEGMENT_7_SEGMENT_N'
           b0110000_1;
33         `SEGMENT_7_INPUT_BITS_N'd15: D=`SEGMENT_7_SEGMENT_N'
           b0111000_1;
34         default: D=`SEGMENT_7_SEGMENT_N'b0111000_1;
35     endcase
36
37 endmodule

```

7-Segment Display Since we can only control one digit of the 7-segment display each time, I design a module that takes the 4-digit patterns as input and shows the 1 digit on the display when the clock raises. Whenever the clock raises, the module will switch the control `d_sel` to different digit and shows the corresponding digit. Take an example, when the first clock raise occur, the module will set `d_sel = 4' b1110` and `d_out = d0`. As for second clock pulse, the module will output `d_sel = 4' b1101` and `d_out = d1` and so on.

```

1  `include "global.v"
2
3  //`define DIGIT_N 4
4  //`define SEGMENT_N 8
5
6
7  module display_7seg(
8      d_sel,
9      d_out,
10     clk,
11     rst,
12     d0,
13     d1,
14     d2,
15     d3
16 );
17
18     output [0:`SEGMENT_7_DISPALY_DIGIT_N-1]d_sel;

```

```

19     output [`SEGMENT_7_SEGMENT_N-1:0]d_out;
20     input  clk;
21     input  rst;
22     input  [`SEGMENT_7_SEGMENT_N-1:0]d0;
23     input  [`SEGMENT_7_SEGMENT_N-1:0]d1;
24     input  [`SEGMENT_7_SEGMENT_N-1:0]d2;
25     input  [`SEGMENT_7_SEGMENT_N-1:0]d3;
26
27     reg [0:`SEGMENT_7_DISPALY_DIGIT_N-1]d_sel;
28     reg [`SEGMENT_7_SEGMENT_N-1:0]d_out;
29     reg [0:`SEGMENT_7_DISPALY_DIGIT_N-1]d_sel_temp;
30     reg [`SEGMENT_7_SEGMENT_N-1:0]d_out_temp;
31     wire clk_out;
32
33     //      initial
34     //      begin
35     //          d_sel <= `SEGMENT_7_DISPALY_DIGIT_N'b1110;
36     //          d_out <= `SEGMENT_7_EMPTY;
37     //      end
38
39     segment7_frequency_divider U0(.clk(clk), .rst(`RST_OFF), .clk_out(
        clk_out));
40
41     always@(d_sel)
42     begin
43         case((d_sel << 1) | (d_sel >> (`SEGMENT_7_DISPALY_DIGIT_N-1)))
44             `SEGMENT_7_DISPALY_DIGIT_N'b1110: d_out_temp <= d0;
45             `SEGMENT_7_DISPALY_DIGIT_N'b1101: d_out_temp <= d1;
46             `SEGMENT_7_DISPALY_DIGIT_N'b1011: d_out_temp <= d2;
47             `SEGMENT_7_DISPALY_DIGIT_N'b0111: d_out_temp <= d3;
48             default: d_out_temp <= `SEGMENT_7_NONE;
49         endcase
50         d_sel_temp <= (d_sel << 1) | (d_sel >> (
            `SEGMENT_7_DISPALY_DIGIT_N-1));
51     end
52
53     always@(posedge clk_out or negedge rst)
54     begin
55         if(~rst)
56         begin
57             d_out <= `SEGMENT_7_EMPTY;
58             d_sel <= `SEGMENT_7_DISPALY_DIGIT_N'b1110;
59         //          d_sel <= d_sel_temp;
60         end
61         else
62         begin
63             d_out <= d_out_temp;
64             d_sel <= d_sel_temp;
65         end
66     end
67

```

68 **endmodule****40-Second Timer**

```

1  include "global.v"
2
3  //`define BCD_COUNTER_BITS 8
4  //`define RST_HIGH 1'b1
5
6  //`define INPUT_BITS_N 4
7  //`define SEGMENT_7_DISPALY_DIGIT_N 4
8  //`define SEGMENT_7_SEGMENT_N 8
9
10 //`define P 4'b1111
11 //`define NONE_SEG7 `SEGMENT_7_SEGMENT_N'b1111111_1
12
13 module prelab(
14     leds,
15     D_SEL,
16     D_OUT,
17     restart,
18     push,
19     rst,
20     clk
21 );
22 output [`LEDS_NUM-1:0] leds;
23 output [`SEGMENT_7_DISPALY_DIGIT_N-1:0] D_SEL;
24 output [`SEGMENT_7_SEGMENT_N-1:0] D_OUT;
25 input restart;
26 input push;
27 input rst;
28 input clk;
29
30 //    reg [`BCD_COUNTER_BITS-1:0] q;
31 wire DIV_CLK;
32 wire [`SEGMENT_7_INPUT_BITS_N-1:0] D1_BINARY;
33 wire [`SEGMENT_7_INPUT_BITS_N-1:0] D2_BINARY;
34 wire [`SEGMENT_7_SEGMENT_N-1:0] D1_SEGMENT7;
35 wire [`SEGMENT_7_SEGMENT_N-1:0] D2_SEGMENT7;
36 wire PAUSE_ONEPULSE;
37 wire RESTART_ONEPULSE;
38 wire IS_PAUSE;
39 wire IS_RESTART;
40
41 wire [`BCD_COUNTER_BITS-1:0] Q;
42
43 //    assign IS_RESTART = 1;
44 //    assign IS_PAUSE = 0;
45     onepulse PauseBtn(.rst(rst), .clk(clk), .push(push), .push_onepulse
        (PAUSE_ONEPULSE));
46     onepulse RestartBtn(.rst(rst), .clk(clk), .push(restart), .

```

```

        push_onepulse(RESTART_ONEPULSE));
47    fsm FSM(.clk(clk), .pause(PAUSE_ONEPULSE), .restart(
        RESTART_ONEPULSE), .is_pause(IS_PAUSE), .is_restart(IS_RESTART))
        ;
48
49    // 2-Digits Binary up counter
50    frequency_divider U0(.clk(clk), .rst(IS_RESTART), .clk_out(DIV_CLK)
        );
51    binary_down_2digit_counter U1(.clk(DIV_CLK), .rst(IS_RESTART), .
        is_pause(IS_PAUSE), .q(Q));
52
53    // LEDs controller
54    led_control LED_CONTROL(.q(Q), .is_pause(IS_PAUSE), .is_restart(
        IS_RESTART), .leds(leds));
55
56    // Extract digits
57    extract U2(.x(Q), .d1(D1_BINARY), .d2(D2_BINARY));
58
59    // Convert binary to 7-segment
60    segment7 U3(.i(D1_BINARY), .D(D1_SEGMENT7));
61    segment7 U4(.i(D2_BINARY), .D(D2_SEGMENT7));
62
63    // Show
64    display_7seg(.clk(clk), .rst(rst), .d0(D1_SEGMENT7), .d1(
        D2_SEGMENT7), .d2(`SEGMENT_7_NONE), .d3(`SEGMENT_7_NONE), .d_sel
        (D_SEL), .d_out(D_OUT));
65 //    display_hex_7seg (.clk(clk), .rst(rst), .d0(D1_BINARY), .d1(
        D2_BINARY));
66 endmodule

```

I/O Pin Assignment

I/O	clk	rst	push	restart	D_SEL[0]	D_SEL[1]	D_SEL[2]	D_SEL[3]
LOC	W5	V17	T17	W19	U2	U4	V4	W4

I/O	D_OUT[0]	D_OUT[1]	D_OUT[2]	D_OUT[3]	D_OUT[4]	D_OUT[5]	D_OUT[6]	D_OUT[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

I/O	leds[0]	leds[1]	leds[2]	leds[3]	leds[4]	leds[5]	leds[6]	leds[7]
LOC	U16	E19	U19	V19	W18	U15	U14	V14

I/O	leds[8]	leds[9]	leds[10]	leds[11]	leds[12]	leds[13]	leds[14]	leds[15]
LOC	V13	V3	W3	U3	P3	N3	P1	L1

Block Diagram

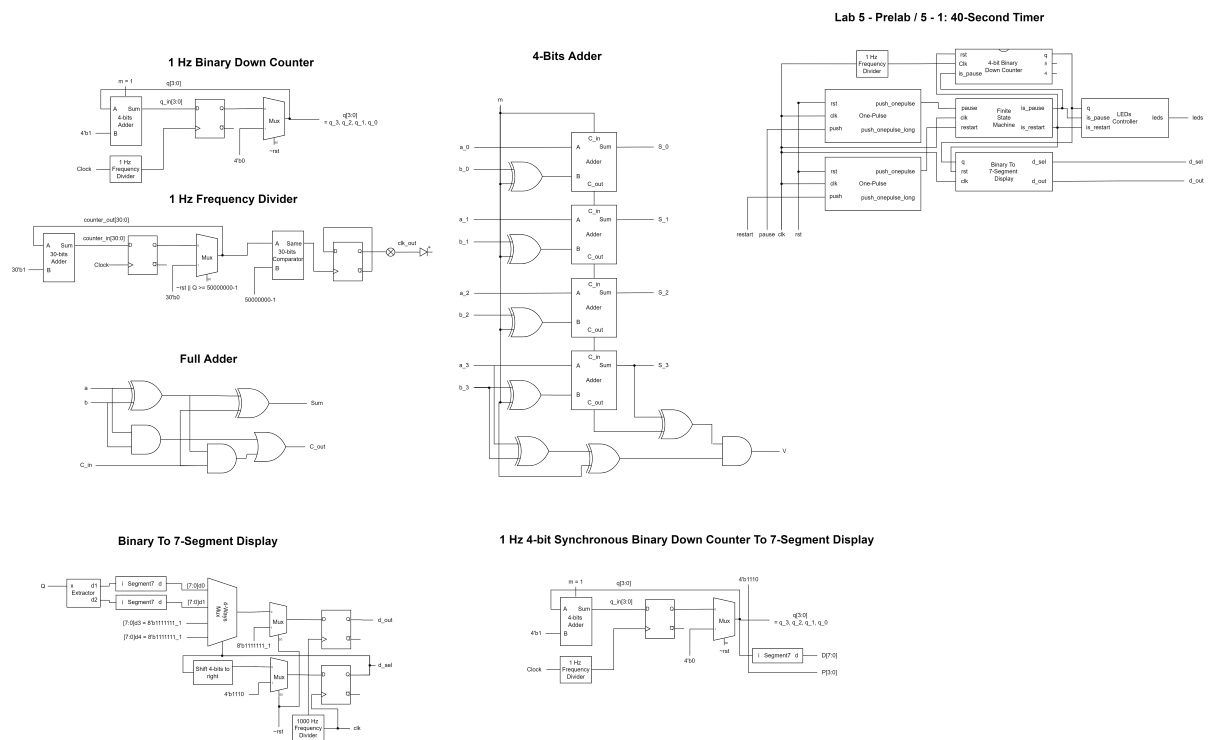


Figure 1: Lab 5-pre Logic Diagram

RTL Simulation

 


Figure 2: Lab 5-pre RTL Simulation

Lab 5-1: 40-Second Down Counter

Because I' ve finished all requirements in the prelab, please refers to the section Lab5-Prelab.

Lab 5 - 2: Stopwatch

Design Specification

Source Code

Debounce

Input: rst, clk, push

Output: push_debounced

One-Pulse

Input: rst, clk, push

Output: push_onepulse

Finite State Machine

Input pause, clk, restart, lap

Output is_pause, is_restart, is_lap

Lap Controller

Output [11:0]q

Input [11:0]i, is_lap

Frequency Divider

Input: rst, clk

Output: clk_out

2-Digit Synchronous Binary Up Counter

Input: rst, clk

Output [11:0]q

LEDs Controller

Input: q, is_pause, is_restart, is_lap

Output: [15:0]leds

Minute-Second Separator

Input [11:0]i

Output [7:0]d0_min, [7:0]d1_min, [7:0]d0_sec, [7:0]d1_sec

Binary To 7-Segment Convertor

Input: [3:0] i

Output: [3:0]P, [7:0]D

7-Segment7 Frequency Divider

Input: clk, rst

Output: clk_out

7-Segment Display

Output: [0:3]d_sel, [7:0]d_out

Input: clk, rst, [7:0]d0, [7:0]d1, [7:0]d2, [7:0]d3

7-Segment Time Display

Output [3:0]d_sel, [7:0]d_out;

Input [11:0]q_lap, clk, rst

Stopwatch

Output [15:0]leds, [3:0]D_SEL, [7:0]D_OUT

Input restart, push, rst, clk

Design Implementation

Global Variables

```

1 // Segment-7 Displayer
2 `define SEGMENT_7_INPUT_BITS_N 4
3 `define SEGMENT_7_DISPALY_DIGIT_N 4
4 `define SEGMENT_7_SEGMENT_N 8
5 `define SEGMENT_7_NONE `SEGMENT_7_SEGMENT_N'b1111111_1
6 `define SEGMENT_7_EMPTY `SEGMENT_7_SEGMENT_N'b1111111_0
7
8 // @Segment-7 Displayer Frequency Divider
9 `define SEGMENT_7_FREQ_DIV_BITS 30
10 // 1000 Hz
11 `define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000
12 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd2
13 // 1 Hz
14 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd5000000
15 `define RST_OFF 1'b1
16
17 // @BCD Counter
18 `define BCD_COUNTER_BITS 12
19 `define BCD_COUNTER_LIMIT `BCD_COUNTER_BITS'd3600
20 `define BCD_COUNTER_ZERO `BCD_COUNTER_BITS'd0
21
22 // @Frequency Divider
23 `define FREQ_DIV_BITS 30
24 // 1 Hz
25 `define FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000000
26 //`define FREQ_DIV_COUNT `FREQ_DIV_BITS'd2
27
28 // @LED control
29 `define LEDS_NUM 16
30
31 // @Minute-Second Seperator
32 `define UNIT_BITS 6
33
34 // One Pulse
35 `define COUNTER_BITS_N 30
36 `define PRESS_CYCLE_N `COUNTER_BITS_N'd200000000
37 //`define PRESS_CYCLE_N `COUNTER_BITS_N'd2

```

Debounce Same as lab 5-Prelab.

One-Pulse It's similar to the `one-pulse` module in lab 5-Prelab. I use a counter to count the clock cycles during the button is pressed. If the counting exceed a threshold, it will trigger a long press pulse `push_onepulse_long`. Otherwise, it will trigger a click pulse `push_onepulse`.

```
1 `include "global.v"
```

```
2
3 //`define LONG_PRESS_N 3
4 //`define COUNTER_BITS_N 30
5
6 module onepulse (
7     rst,
8     clk,
9     clk_long,
10    push,
11    push_onepulse,
12    push_onepulse_long,
13    push_debounced,
14    push_sig,
15    push_sig_long
16);
17
18    input clk, clk_long, rst;
19    input push;
20    output push_onepulse;
21    output push_onepulse_long;
22    output push_debounced;
23    output push_sig;
24    output push_sig_long;
25    // internal registers
26    reg push_onepulse_next;
27    reg push_debounced_delay;
28    reg push_onepulse;
29
30    reg push_onepulse_next_long;
31    reg push_debounced_delay_long;
32    reg push_onepulse_long;
33
34    reg [`COUNTER_BITS_N-1:0]counter_temp;
35    reg [`COUNTER_BITS_N-1:0]counter;
36    reg push_sig;
37    reg push_sig_long;
38
39    debounce U0(.clk(clk), .rst(rst), .push(push), .push_debounced(
40        push_debounced));
41    //    debounce U1(.clk(clk_long), .rst(rst), .push(push), .
42        push_debounced(push_debounced_long));
43
44    initial begin
45        push_onepulse = 1'b0;
46        push_onepulse_long = 1'b0;
47    end
48
49    always@(*) begin
50        push_onepulse = push_sig;
51        push_onepulse_long = push_sig_long;
52    end
53
```

```

51
52 // Switching long or short
53 always@(counter) begin
54     counter_temp <= counter + `COUNTER_BITS_N'b1;
55 end
56
57 always @(posedge clk or negedge rst) begin
58     if (~rst) begin
59         counter <= `COUNTER_BITS_N'b0;
60         push_sig_long <= 1'b0;
61         push_sig <= 1'b0;
62     end else if(~push_debounced) begin
63         if(counter > `PRESS_CYCLE_N) begin
64             push_sig <= 1'b0;
65             push_sig_long <= 1'b1;
66         end else if(counter > 0) begin
67             push_sig <= 1'b1;
68             push_sig_long <= 1'b0;
69         end else begin
70             push_sig <= 1'b0;
71             push_sig_long <= 1'b0;
72         end
73         counter <= `COUNTER_BITS_N'b0;
74     end else if(push_debounced) begin
75         counter <= counter_temp;
76         push_sig <= 1'b0;
77         push_sig_long <= 1'b0;
78     end
79 end
80 endmodule

```

Finite State Machine It's similar to the finite state machine in the Lab 5-Prelab. I just add a new control signal `is_lap`. Whenever the button `lap` is clicked, the signal `is_lap` will be inverted.

```

1 `define STATE_LAP 2
2 `define STATE_PAUSE 1
3 `define STATE_START 0
4
5 module fsm(
6     is_pause,
7     is_restart,
8     is_lap,
9     clk,
10    pause,
11    restart,
12    lap
13 );
14
15 output is_pause;

```

```
16     output is_restart;
17     output is_lap;
18     input clk;
19     input pause;
20     input restart;
21     input lap;
22
23     reg is_lap;
24     reg is_restart;
25     reg is_pause;
26     reg state;
27
28     initial begin
29         state = `STATE_START;
30     end
31
32     always@(posedge restart) begin
33         is_restart <= is_restart ^ 1;
34     end
35
36     always@(posedge lap) begin
37         is_lap <= ~is_lap;
38     end
39
40     always@(posedge pause) begin
41         if(state == `STATE_PAUSE) begin
42             state = `STATE_START;
43             is_pause = 0;
44         end
45         else if(state == `STATE_START) begin
46             state = `STATE_PAUSE;
47             is_pause = 1;
48         end
49     end
50 endmodule
```

Lap Controller In stopwatch, we need to freeze the display in the lap. The lap controller will stop updating the latest counting while `is_lap` is `true`.

```
1  `include "global.v"
2
3  module lap_controller(
4      q,
5      i,
6      is_lap
7  );
8
9      output [`BCD_COUNTER_BITS-1:0]q;
10     input  [`BCD_COUNTER_BITS-1:0]i;
```

```
11     input is_lap;
12
13     reg [`BCD_COUNTER_BITS-1:0]q;
14
15     initial begin
16         q <= i;
17     end
18
19     always@(is_lap or i) begin
20         if(!is_lap) begin
21             q <= i;
22         end
23     end
24 endmodule
```

Frequency Divider Same as lab 5-Prelab

2-Digit Synchronous Binary Up Counter It's similar to the down counter in the Lab 5-Prelab. The only different thing is this counter counts up rather than down.

```
1  `include "global.v"
2
3  module binary_up_4digit_counter(
4      q,
5      clk,
6      rst,
7      is_pause
8  );
9
10     output [`BCD_COUNTER_BITS-1:0]q;
11     input clk;
12     input rst;
13     input is_pause;
14
15     reg [`BCD_COUNTER_BITS-1:0]q;
16     reg [`BCD_COUNTER_BITS-1:0]q_in;
17
18     initial
19     begin
20         // q <= `BCD_COUNTER_LIMIT;
21         q <= `BCD_COUNTER_ZERO;
22     end
23
24     always@(q or is_pause)
25     begin
26         // if(q == (`BCD_COUNTER_LIMIT - `BCD_COUNTER_BITS'd1))
27         if(q >= `BCD_COUNTER_LIMIT)
28             begin
```



```
29 //          q_in <= `BCD_COUNTER_ZERO;
30          q_in <= `BCD_COUNTER_LIMIT;
31      end
32      else
33      begin
34          if(~is_pause)
35          begin
36              q_in <= q + `BCD_COUNTER_BITS'd1;
37          end
38          else
39          begin
40              q_in <= q;
41          end
42      end
43  end
44
45  always@(posedge clk or negedge rst)
46  begin
47      if(~rst)
48      begin
49          //          q <= `BCD_COUNTER_LIMIT;
50              q <= `BCD_COUNTER_ZERO;
51          end
52          else
53          begin
54              q <= q_in;
55          end
56      end
57  endmodule
```

LEDs Controller It's similar to the LEDs controller in the Lab 5-Prelab. The LEDs will all light up while the counter hit the limit. On the other hand, while the counter is counting, `leds[0]` will be turned on. While the stopwatch enters a lap, `leds[1]` will be turned on.

```
1  `include "global.v"
2
3  module led_control(
4      q,
5      is_pause,
6      is_restart,
7      is_lap,
8      leds
9  );
10
11  input  [`BCD_COUNTER_BITS-1:0]q;
12  input  is_pause;
13  input  is_restart;
14  input  is_lap;
15  output [`LEDS_NUM-1:0]leds;
```

```

16
17     reg [`LEDS_NUM-1:0] leds;
18
19     always@(q or is_pause or is_restart or is_lap) begin
20         if(q == `BCD_COUNTER_LIMIT) begin
21             leds = [`LEDS_NUM{1'b1}];
22         end else begin
23             leds[`LEDS_NUM-1:2] = {(`LEDS_NUM-2){1'b0}};
24             if((!is_pause) && (is_restart)) begin
25                 leds[0] = 1'b1;
26             end else begin
27                 leds[0] = 1'b0;
28             end
29
30             if(is_lap) begin
31                 leds[1] = 1'b1;
32             end else begin
33                 leds[1] = 1'b0;
34             end
35         end
36     end
37 endmodule

```

Minute-Second Separator This module converts the time in seconds to the form of minutes and seconds. I extract the minute unit with dividing to 60 and the seconds unit with taking the modulo to 60. Finally, we can separate the digits with similar ways.

```

1  `include "global.v"
2
3  module min_sec_separate(
4      i,
5      d0_min,
6      d1_min,
7      d0_sec,
8      d1_sec
9  );
10
11     input  [`BCD_COUNTER_BITS-1:0] i;
12     output [`SEGMENT_7_INPUT_BITS_N-1:0] d0_min;
13     output [`SEGMENT_7_INPUT_BITS_N-1:0] d1_min;
14     output [`SEGMENT_7_INPUT_BITS_N-1:0] d0_sec;
15     output [`SEGMENT_7_INPUT_BITS_N-1:0] d1_sec;
16
17     wire  [`BCD_COUNTER_BITS-1:0] MINS;
18     wire  [`BCD_COUNTER_BITS-1:0] SECS;
19     wire  [`BCD_COUNTER_BITS-1:0] D0_MIN;
20     wire  [`BCD_COUNTER_BITS-1:0] D1_MIN;
21     wire  [`BCD_COUNTER_BITS-1:0] D0_SEC;
22     wire  [`BCD_COUNTER_BITS-1:0] D1_SEC;

```

```

23
24     assign MINS = i / 60;
25     assign SECS = i % 60;
26
27     assign D0_MIN = MINS % 10;
28     assign D1_MIN = MINS / 10;
29     assign D0_SEC = SECS % 10;
30     assign D1_SEC = SECS / 10;
31
32     assign d0_min = D0_MIN[`SEGMENT_7_INPUT_BITS_N-1:0];
33     assign d1_min = D1_MIN[`SEGMENT_7_INPUT_BITS_N-1:0];
34     assign d0_sec = D0_SEC[`SEGMENT_7_INPUT_BITS_N-1:0];
35     assign d1_sec = D1_SEC[`SEGMENT_7_INPUT_BITS_N-1:0];
36 endmodule

```

Binary To 7-Segment Convertor Same as lab 5-Prelab

7-Segment Display Same as lab 5-Prelab

7-Segment Time Display This module shows the time on the 7-segment display. It takes seconds as input and output the control signals of the 7-segment display. We can implement this specialty with the modules `Minute-Second Separator`, `Binary To 7-Segment Convertor`, and `7-Segment Display`. First, I parse the time in second to the form of minutes and seconds. Then, convert them into the patterns shown on the 7-segment display.

```

1  `include "global.v"
2
3  module display_time_7_segment(
4      d_sel,
5      d_out,
6      q_lap,
7      clk,
8      rst
9  );
10
11     output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]d_sel;
12     output [`SEGMENT_7_SEGMENT_N-1:0]d_out;
13     input  [`BCD_COUNTER_BITS-1:0]q_lap;
14     input  clk;
15     input  rst;
16
17     wire  [`SEGMENT_7_INPUT_BITS_N-1:0]D0_MIN_BINARY;
18     wire  [`SEGMENT_7_INPUT_BITS_N-1:0]D1_MIN_BINARY;
19     wire  [`SEGMENT_7_INPUT_BITS_N-1:0]D0_SEC_BINARY;
20     wire  [`SEGMENT_7_INPUT_BITS_N-1:0]D1_SEC_BINARY;
21     wire  [`SEGMENT_7_SEGMENT_N-1:0]D0_MIN_SEGMENT7;

```

```

22  wire [`SEGMENT_7_SEGMENT_N-1:0]D1_MIN_SEGMENT7;
23  wire [`SEGMENT_7_SEGMENT_N-1:0]D0_SEC_SEGMENT7;
24  wire [`SEGMENT_7_SEGMENT_N-1:0]D1_SEC_SEGMENT7;
25
26  // Extract digits
27  min_sec_separate SEP(.i(q_lap), .d0_min(D0_MIN_BINARY), .d1_min(
    D1_MIN_BINARY), .d0_sec(D0_SEC_BINARY), .d1_sec(D1_SEC_BINARY));
28
29  // Convert binary to 7-segment
30  segment7 D0_MIN_CONV(.i(D0_MIN_BINARY), .D(D0_MIN_SEGMENT7));
31  segment7 D1_MIN_CONV(.i(D1_MIN_BINARY), .D(D1_MIN_SEGMENT7));
32  segment7 D0_SEC_CONV(.i(D0_SEC_BINARY), .D(D0_SEC_SEGMENT7));
33  segment7 D1_SEC_CONV(.i(D1_SEC_BINARY), .D(D1_SEC_SEGMENT7));
34
35  // Show
36  display_7seg(.clk(clk), .rst(rst), .d0(D0_SEC_SEGMENT7), .d1(
    D1_SEC_SEGMENT7), .d2(D0_MIN_SEGMENT7), .d3(D1_MIN_SEGMENT7), .
    d_sel(d_sel), .d_out(d_out));
37  endmodule

```

Stopwatch To implement a stopwatch, I only need to combine all modules into one. The **Frequency Divider** generate 1 Hz clock to trigger the **2-Digit Synchronous Binary Up Counter**. The **One-Pulse** module send signal whenever the button is clicked or long pressed to control the **Finite State Machine**. The **Lap Controller** controls the number shown on the display by the module **7-Segment Time Display**.

```

1  `include "global.v"
2
3  module exp_2(
4      leds,
5      D_SEL,
6      D_OUT,
7      restart,
8      push,
9      rst,
10     clk
11 );
12 output [`LEDS_NUM-1:0]leds;
13 output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]D_SEL;
14 output [`SEGMENT_7_SEGMENT_N-1:0]D_OUT;
15 input restart;
16 input push;
17 input rst;
18 input clk;
19
20 // reg [`BCD_COUNTER_BITS-1:0]q;
21 wire DIV_CLK;
22 wire [`SEGMENT_7_INPUT_BITS_N-1:0]D0_MIN_BINARY;

```

```

23  wire [`SEGMENT_7_INPUT_BITS_N-1:0]D1_MIN_BINARY;
24  wire [`SEGMENT_7_INPUT_BITS_N-1:0]D0_SEC_BINARY;
25  wire [`SEGMENT_7_INPUT_BITS_N-1:0]D1_SEC_BINARY;
26  wire [`SEGMENT_7_SEGMENT_N-1:0]D0_MIN_SEGMENT7;
27  wire [`SEGMENT_7_SEGMENT_N-1:0]D1_MIN_SEGMENT7;
28  wire [`SEGMENT_7_SEGMENT_N-1:0]D0_SEC_SEGMENT7;
29  wire [`SEGMENT_7_SEGMENT_N-1:0]D1_SEC_SEGMENT7;
30
31  wire PAUSE_ONEPULSE;
32  wire RESTART_ONEPULSE;
33  wire LAP_ONEPULSE;
34  wire IS_PAUSE;
35  wire IS_RESTART;
36  wire IS_LAP;
37
38  wire [`BCD_COUNTER_BITS-1:0]Q;
39  wire [`BCD_COUNTER_BITS-1:0]Q_LAP;
40
41  // assign IS_RESTART = 1;
42  // assign IS_PAUSE = 0;
43
44  // 1 Hz Clock
45  frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));
46
47  onepulse PauseBtn(.rst(rst), .clk(clk), .clk_long(DIV_CLK), .push(
    push), .push_onepulse(PAUSE_ONEPULSE));
48  onepulse RestartBtn(.rst(rst), .clk(clk), .clk_long(DIV_CLK), .push(
    restart), .push_onepulse(LAP_ONEPULSE), .push_onepulse_long(
    RESTART_ONEPULSE));
49  fsm FSM(.clk(clk), .pause(PAUSE_ONEPULSE), .restart(
    RESTART_ONEPULSE), .lap(LAP_ONEPULSE), .is_pause(IS_PAUSE), .
    is_restart(IS_RESTART), .is_lap(IS_LAP));
50
51  // 2-Digits Binary up counter
52  binary_up_4digit_counter U1(.clk(DIV_CLK), .rst(IS_RESTART), .
    is_pause(IS_PAUSE), .q(Q));
53  lap_controller LAP_CONTROL(.q(Q_LAP), .i(Q), .is_lap(IS_LAP));
54
55  // LEDs controller
56  led_control LED_CONTROL(.q(Q), .is_pause(IS_PAUSE), .is_restart(
    IS_RESTART), .is_lap(IS_LAP), .leds(leds));
57  display_time_7_segment TIME_DISPLAY(.q_lap(Q_LAP), .clk(clk), .rst(
    rst), .d_sel(D_SEL), .d_out(D_OUT));
58  endmodule

```

I/O Pin Assignment


I/O	clk	rst	push	restart	D_SEL[0]	D_SEL[1]	D_SEL[2]	D_SEL[3]
LOC	W5	V17	T17	W19	U2	U4	V4	W4

I/O	D_OUT[0]	D_OUT[1]	D_OUT[2]	D_OUT[3]	D_OUT[4]	D_OUT[5]	D_OUT[6]	D_OUT[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

I/O	leds[0]	leds[1]	leds[2]	leds[3]	leds[4]	leds[5]	leds[6]	leds[7]
LOC	U16	E19	U19	V19	W18	U15	U14	V14

I/O	leds[8]	leds[9]	leds[10]	leds[11]	leds[12]	leds[13]	leds[14]	leds[15]
LOC	V13	V3	W3	U3	P3	N3	P1	L1

Binary Time To 7-Segment Display

 

The block diagram illustrates a digital circuit for a lap counter and LED display. The inputs are `restart`, `pause`, `clk`, and `rst`. The circuit consists of the following blocks and their interconnections:

- 1 Hz Frequency Divider**: Receives `clk` and provides a `1 Hz` signal to the `push_onepulse` and `push_onepulse_long` blocks.
- push_onepulse (One-Pulse)**: Receives `rst`, `clk`, and `push`. It outputs `is_pause` and `is_restart` to the `Finite State Machine` and `Lap Controller`.
- push_onepulse_long (One-Pulse)**: Receives `rst`, `clk`, and `push`. It outputs `is_lap` to the `Finite State Machine` and `Lap Controller`.
- 4-bit Binary Up Counter**: Receives `rst`, `clk`, and `is_pause`. It outputs a 4-bit binary value `q` to the `Finite State Machine` and `Lap Controller`.
- Finite State Machine**: Receives `clk`, `pause`, `restart`, `lap`, `is_pause`, `is_restart`, and `is_lap`. It outputs `q` to the `Lap Controller` and `LEDs Controller`.
- Lap Controller**: Receives `is_lap` and `q`. It outputs `q` to the `LEDs Controller`.
- `LEDs Controller`: Receives `q`, `is_pause`, `is_restart`, and `is_lap`. It outputs `leds` (7-bit) to the `LEDs`.
- `Binary Time To 7-Segment Display`: Receives `q`, `rst`, and `clk`. It outputs `d_sel` and `d_out` to the `7-Segment Display`.

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

RTL Simulation

 


Figure 4: Lab 5-2 RTL Simulation

Lab 5 - 3: Timer

Design Specification

Source Code

Debounce

Input: rst, clk, push

Output: push_debounced

One-Pulse

Input: rst, clk, push

Output: push_onepulse

Finite State Machine

Output is_pause, is_restart, is_setting, [11:0]q_target

Input clk, pause, restart, mode_switch

Frequency Divider

Input: rst, clk

Output: clk_out

2-Digit Synchronous Binary Down Counter

Input: rst, clk

Output [11:0]q

LEDs Controller

Input: q, is_pause, is_restart, is_lap

Output: [15:0]leds

Minute-Second Separator

Input [11:0]i

Output [7:0]d0_min, [7:0]d1_min, [7:0]d0_sec, [7:0]d1_sec

Binary To 7-Segment Convertor

Input: [3:0] i

Output: [3:0]P, [7:0]D

7-Segment7 Frequency Divider

Input: clk, rst

Output: clk_out

7-Segment Display

Output: [0:3]d_sel, [7:0]d_out

Input: clk, rst, [7:0]d0, [7:0]d1, [7:0]d2, [7:0]d3

7-Segment Time Display

Output [3:0]d_sel, [7:0]d_out;

Input [11:0]q_lap, clk, rst

Timer

Output [15:0]leds, [3:0]D_SEL, [7:0]D_OUT

Input restart, push, rst, clk

Design Implementation

Global Variables

```
1 // Segment-7 Displayer
2 `define SEGMENT_7_INPUT_BITS_N 4
3 `define SEGMENT_7_DISPALY_DIGIT_N 4
4 `define SEGMENT_7_SEGMENT_N 8
5 `define SEGMENT_7_NONE `SEGMENT_7_SEGMENT_N'b1111111_1
6 `define SEGMENT_7_EMPTY `SEGMENT_7_SEGMENT_N'b1111111_0
```

```

7
8 // @Segment-7 Displayer Frequency Divider
9 `define SEGMENT_7_FREQ_DIV_BITS 30
10 // 1000 Hz
11 `define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000
12 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd2
13 // 1 Hz
14 //`define SEGMENT_7_FREQ_DIV_COUNT `FREQ_DIV_BITS'd5000000
15 `define RST_OFF 1'b1
16
17 // @BCD Counter
18 `define BCD_COUNTER_BITS 12
19 `define BCD_COUNTER_LIMIT `BCD_COUNTER_BITS'd60
20 `define BCD_COUNTER_ZERO `BCD_COUNTER_BITS'd0
21
22 // @Frequency Divider
23 `define FREQ_DIV_BITS 30
24 // 1 Hz
25 `define FREQ_DIV_COUNT `FREQ_DIV_BITS'd50000000
26 //`define FREQ_DIV_COUNT `FREQ_DIV_BITS'd2
27
28 // @LED control
29 `define LEDS_NUM 16
30
31 // @Minute-Second Seperator
32 `define UNIT_BITS 6
33
34 // One Pulse
35 `define COUNTER_BITS_N 30
36 `define PRESS_CYCLE_N `COUNTER_BITS_N'd200000000
37 //`define PRESS_CYCLE_N `COUNTER_BITS_N'd2

```

Debounce Same as lab 5-Prelab.

One-Pulse Same as lab 5-2.

Finite State Machine The finite state machine controls 3 signals: `is_pause`, `is_setting` and `is_restart`. The down counter will pause while the signal `is_pause` is at high voltage and resume to count while the signal is at low voltage. It is controlled independently, so I only need to inverse the signal whenever the button `restart` is pressed.

On the other hand, the down counter will reset to 0 when the signal `is_restart` raises. It only depends on `restart` button, so we only need to inverse the signal whenever the button is clicked.

Similarly, the signal `is_setting` indicates whether we can set the timer or not. It's controlled by the DIP switch directly.

To set up the timer limit, I use 2 always loop to detect the button. One is for minutes and the other is for seconds. They count the click of each button independently. Then, I sum them up together as the output.

```
1  `include "global.v"
2
3  `define STATE_SETTING 2
4  `define STATE_PAUSE 1
5  `define STATE_START 0
6
7  module fsm(
8      is_pause,
9      is_restart,
10     is_setting,
11     q_target,
12     pause_trig,
13     restart_trig,
14     clk,
15     pause,
16     restart,
17     mode_switch
18 );
19
20     output is_pause;
21     output is_restart;
22     output is_setting;
23     output [`BCD_COUNTER_BITS-1:0]q_target;
24     output restart_trig;
25     output pause_trig;
26     input clk;
27     input pause;
28     input restart;
29     input mode_switch;
30
31     reg is_restart, is_restart_temp;
32     reg is_pause, is_pause_temp;
33     reg state, state_temp;
34     reg [`BCD_COUNTER_BITS-1:0]q_target;
35     reg [`BCD_COUNTER_BITS-1:0]q_target_min;
36     reg [`BCD_COUNTER_BITS-1:0]q_target_sec;
37     // reg last_restart;
38     // reg last_pause;
39
40     assign is_setting = mode_switch;
41
42     initial begin
43         q_target = `BCD_COUNTER_BITS'd0;
44         // last_state = `STATE_START;
45         state = `STATE_START;
46         state_temp = `STATE_START;
```

```
47
48     is_restart = 1'b0;
49     is_restart_temp = 1'b0;
50     is_pause = 1'b0;
51     is_pause_temp = 1'b0;
52 //     last_restart = 1'b0;
53 //     last_is_pause = 1'b0;
54 //     last_pause = 1'b0;
55
56     q_target_min = `BCD_COUNTER_BITS'd0;
57     q_target_sec = `BCD_COUNTER_BITS'd0;
58 end
59
60 always@(posedge restart) begin
61     if(!mode_switch) begin
62         is_restart_temp <= is_restart ^ 1;
63     end
64 end
65
66 always@(posedge pause) begin
67     if(!mode_switch) begin
68         if(state == `STATE_PAUSE) begin
69 //             last_state <= state;
70 //             last_is_pause <= is_pause;
71
72             state_temp <= `STATE_START;
73             is_pause_temp <= 0;
74         end else if(state == `STATE_START) begin
75 //             last_state <= state;
76 //             last_is_pause <= is_pause;
77
78             state_temp <= `STATE_PAUSE;
79             is_pause_temp <= 1;
80         end else begin
81             state_temp <= `STATE_START;
82             is_pause_temp <= 1'b0;
83
84 //             last_state <= `STATE_SETTING;
85 //             last_is_pause <= 0;
86         end
87     end
88 end
89
90 always@(posedge clk) begin
91 //     is_restart <= is_restart_temp;
92     q_target <= q_target_min + q_target_sec;
93
94     if(mode_switch) begin
95         state <= `STATE_SETTING;
96         is_pause <= 0;
97         is_restart <= 1'b1;
```

```

98         end else begin
99             state <= state_temp;
100             is_pause <= is_pause_temp;
101             is_restart <= is_restart_temp;
102         end
103     end
104
105     always@(posedge restart) begin
106         if(mode_switch) begin
107             q_target_min <= q_target_min + `BCD_COUNTER_BITS'd60;
108         end
109     end
110
111     always@(posedge pause) begin
112         if(mode_switch) begin
113             q_target_sec <= q_target_sec + `BCD_COUNTER_BITS'd1;
114         end
115     end
116
117     // always@(posedge pause or mode_switch) begin
118     //     if(mode_switch) begin
119     //         state <= `STATE_SETTING;
120     //         is_pause <= 0;
121     //     end else if(state == `STATE_PAUSE) begin
122     //         state <= `STATE_START;
123     //         is_pause <= 0;
124     //     end else if(state == `STATE_START) begin
125     //         state <= `STATE_PAUSE;
126     //         is_pause <= 1;
127     //     end
128     // end
129 endmodule

```

Frequency Divider Same as lab 5-2.

2-Digit Synchronous Binary Down Counter Same as lab 5-2

LEDs Controller It's similar to the `LEDs controller` in Lab5-2. While we are setting up the timer, `leds[1]` lights up. While the counter is counting, "leds[0] is bright. Whenever the counter hits 0, all the LEDs light up.

```

1  `include "global.v"
2
3  module led_controller(
4      q,
5      is_pause,

```

```

6     is_restart,
7     is_setting,
8     leds
9 );
10
11    input  [`BCD_COUNTER_BITS-1:0]q;
12    input  is_pause;
13    input  is_restart;
14    input  is_setting;
15    output [`LEDS_NUM-1:0]leds;
16
17    reg  [`LEDS_NUM-1:0]leds;
18
19    always@(q or is_pause or is_restart or is_setting) begin
20        if(is_setting) begin
21            leds[`LEDS_NUM-1:2] = {(`LEDS_NUM-2){1'b0}};
22            leds[1] = 1'b1;
23            leds[0] = 1'b0;
24        end else begin
25            if(q == `BCD_COUNTER_ZERO)begin
26                leds = {`LEDS_NUM{1'b1}};
27            end else begin
28                leds[`LEDS_NUM-1:1] = {(`LEDS_NUM-1){1'b0}};
29
30                if((!is_pause) && (is_restart)) begin
31                    leds[0] = 1'b1;
32                end else begin
33                    leds[0] = 1'b0;
34                end
35            end
36        end
37    end
38 endmodule

```

Minute-Second Separator Same as lab 5-2

Binary To 7-Segment Convertor Same as lab 5-Prelab

7-Segment Display Same as lab 5-Prelab

7-Segment Time Display Same as lab 5-2

Timer Combine all the module listed above. **One-Pulse** trigger the **Finite State Machine** and then affect the 3 signal **IS_PAUSE**, **IS_RESTART**, and **IS_SETTING**. These 3 signals control the be-

haviors of Timer Controller and LED Controller and decide the showing of the display and the LEDs.

```

1  `include "global.v"
2
3  module exp_3(
4      leds,
5      D_SEL,
6      D_OUT,
7      restart,
8      push,
9      mode_switch,
10     rst,
11     clk
12 );
13 output [`LEDS_NUM-1:0]leds;
14 output [`SEGMENT_7_DISPALY_DIGIT_N-1:0]D_SEL;
15 output [`SEGMENT_7_SEGMENT_N-1:0]D_OUT;
16 input restart;
17 input push;
18 input mode_switch;
19 input rst;
20 input clk;
21
22 //     reg [`BCD_COUNTER_BITS-1:0]q;
23 wire DIV_CLK;
24 wire [`SEGMENT_7_INPUT_BITS_N-1:0]D0_MIN_BINARY;
25 wire [`SEGMENT_7_INPUT_BITS_N-1:0]D1_MIN_BINARY;
26 wire [`SEGMENT_7_INPUT_BITS_N-1:0]D0_SEC_BINARY;
27 wire [`SEGMENT_7_INPUT_BITS_N-1:0]D1_SEC_BINARY;
28 wire [`SEGMENT_7_SEGMENT_N-1:0]D0_MIN_SEGMENT7;
29 wire [`SEGMENT_7_SEGMENT_N-1:0]D1_MIN_SEGMENT7;
30 wire [`SEGMENT_7_SEGMENT_N-1:0]D0_SEC_SEGMENT7;
31 wire [`SEGMENT_7_SEGMENT_N-1:0]D1_SEC_SEGMENT7;
32
33 wire PAUSE_ONEPULSE;
34 wire RESTART_ONEPULSE;
35 wire IS_PAUSE;
36 wire IS_RESTART;
37 wire IS_SETTING;
38
39 wire [`BCD_COUNTER_BITS-1:0]Q;
40 wire [`BCD_COUNTER_BITS-1:0]Q_SHOW;
41 wire [`BCD_COUNTER_BITS-1:0]Q_TARGET;
42
43 //     assign IS_RESTART = 1;
44 //     assign IS_PAUSE = 0;
45
46 //     assign Q_TARGET = `BCD_COUNTER_BITS'd70;
47
48 // 1 Hz Clock

```

```

49     frequency_divider U0(.clk(clk), .rst(rst), .clk_out(DIV_CLK));
50
51     onepulse PauseBtn(.rst(rst), .clk(clk), .push(push), .push_onepulse
        (PAUSE_ONEPULSE));
52     onepulse RestartBtn(.rst(rst), .clk(clk), .push(restart), .
        push_onepulse(RESTART_ONEPULSE));
53     fsm FSM(.clk(clk), .mode_switch(mode_switch), .pause(PAUSE_ONEPULSE
        ), .restart(RESTART_ONEPULSE), .is_pause(IS_PAUSE), .is_restart(
        IS_RESTART), .is_setting(IS_SETTING), .q_target(Q_TARGET));
54
55     // 2-Digits Binary up counter
56     binary_down_4digit_counter U1(.clk(DIV_CLK), .rst(IS_RESTART), .
        counter_limit(Q_TARGET), .is_pause(IS_PAUSE), .q(Q));
57     timer_controller TIMER_CONTROL(.counting(Q), .target(Q_TARGET), .
        is_setting(IS_SETTING), .q_show(Q_SHOW));
58
59     // LEDs controller
60     led_controller LED_CONTROL(.q(Q), .is_pause(IS_PAUSE), .is_restart(
        IS_RESTART), .is_setting(IS_SETTING), .leds(leds));
61     display_time_7_segment TIME_DISPLAY(.q_show(Q_SHOW), .clk(clk), .
        rst(rst), .d_sel(D_SEL), .d_out(D_OUT));
62 endmodule

```

I/O Pin Assignment

I/O	clk	rst	push	restart	D_SEL[0]	D_SEL[1]	D_SEL[2]	D_SEL[3]
LOC	W5	V17	T17	W19	U2	U4	V4	W4

I/O	D_OUT[0]	D_OUT[1]	D_OUT[2]	D_OUT[3]	D_OUT[4]	D_OUT[5]	D_OUT[6]	D_OUT[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

I/O	leds[0]	leds[1]	leds[2]	leds[3]	leds[4]	leds[5]	leds[6]	leds[7]
LOC	U16	E19	U19	V19	W18	U15	U14	V14

I/O	leds[8]	leds[9]	leds[10]	leds[11]	leds[12]	leds[13]	leds[14]	leds[15]
LOC	V13	V3	W3	U3	P3	N3	P1	L1

Block Diagram

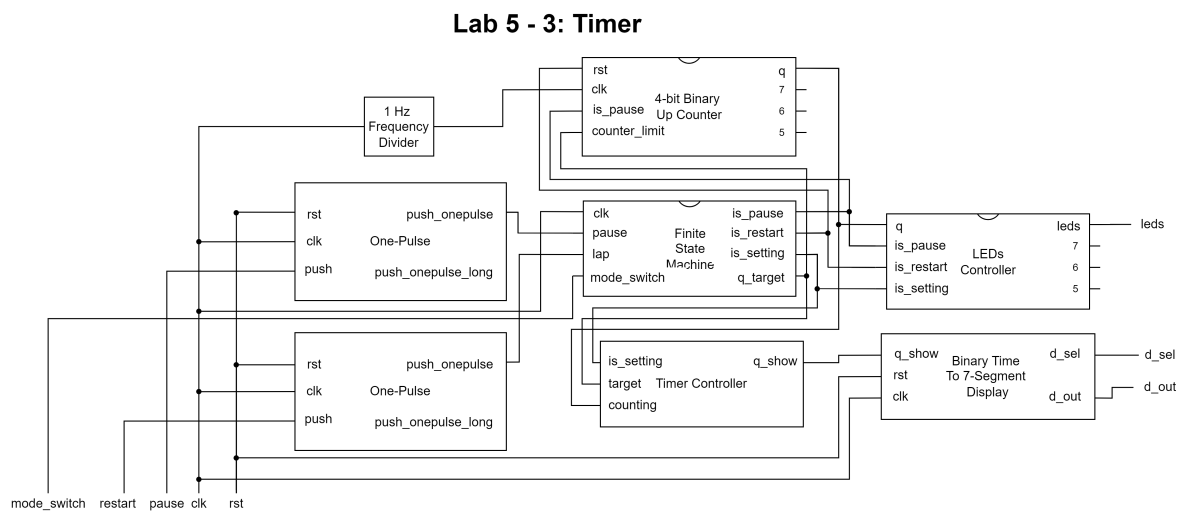


Figure 5: Lab 5-3 Logic Diagram

RTL Simulation

 


Figure 6: Lab 5-3 RTL Simulation

Discussion

In lab 5-2, it took me lots of time to design the state machine because the always block cannot be activated by 2 edge-triggered variables. Finally, I store the variables in the 2 independent variables and add them together as the clock raises. In addition, when I implement the one-pulse module, it took me much time to detect long press and click in the mean time. In the end, I use a counter to count the clock cycle during the pressed button.

Conclusion

The lab5 is much more difficult than previous labs. We' ve learned how to design a more complex circuit with the concept of state machine. We also gradually get used to a larger project.

Reference

- None