

Lab 1 - Verilog Report

106033233 資工大四 周聖諺

Lab 1 - 1: 4-Bit Binary-To-Gray-Code Converter

Design Specification

Source Code

Input: a, b, c, d

Output: w, x, y, z

Design Implementation

First, we can observe that the MSB of the Gray code and binary code are always the same so it doesn't need any conversion. The Boolean equation is $a = w$

In addition, if you list the table of the conversion from 4-bit Gray-code to binary code, you can observe that $a \oplus b = x$, $b \oplus c = y$ and, $c \oplus d = z$. Thus, we can design the circuit as the following code.

Boolean Equation:

$$a = w$$

$$a \oplus b = x$$

$$b \oplus c = y$$

$$c \oplus d = z$$

BCD to Gray Code Truth Table

Decimal	Binary Code (abcd)	Gray Code (wxyz)
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010

Decimal	Binary Code (abcd)	Gray Code (wxyz)
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1100
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000


Verilog Code

```


assign w = a;
assign x = a ^ b;
assign y = b ^ c;
assign z = c ^ d;

```

Block Diagram

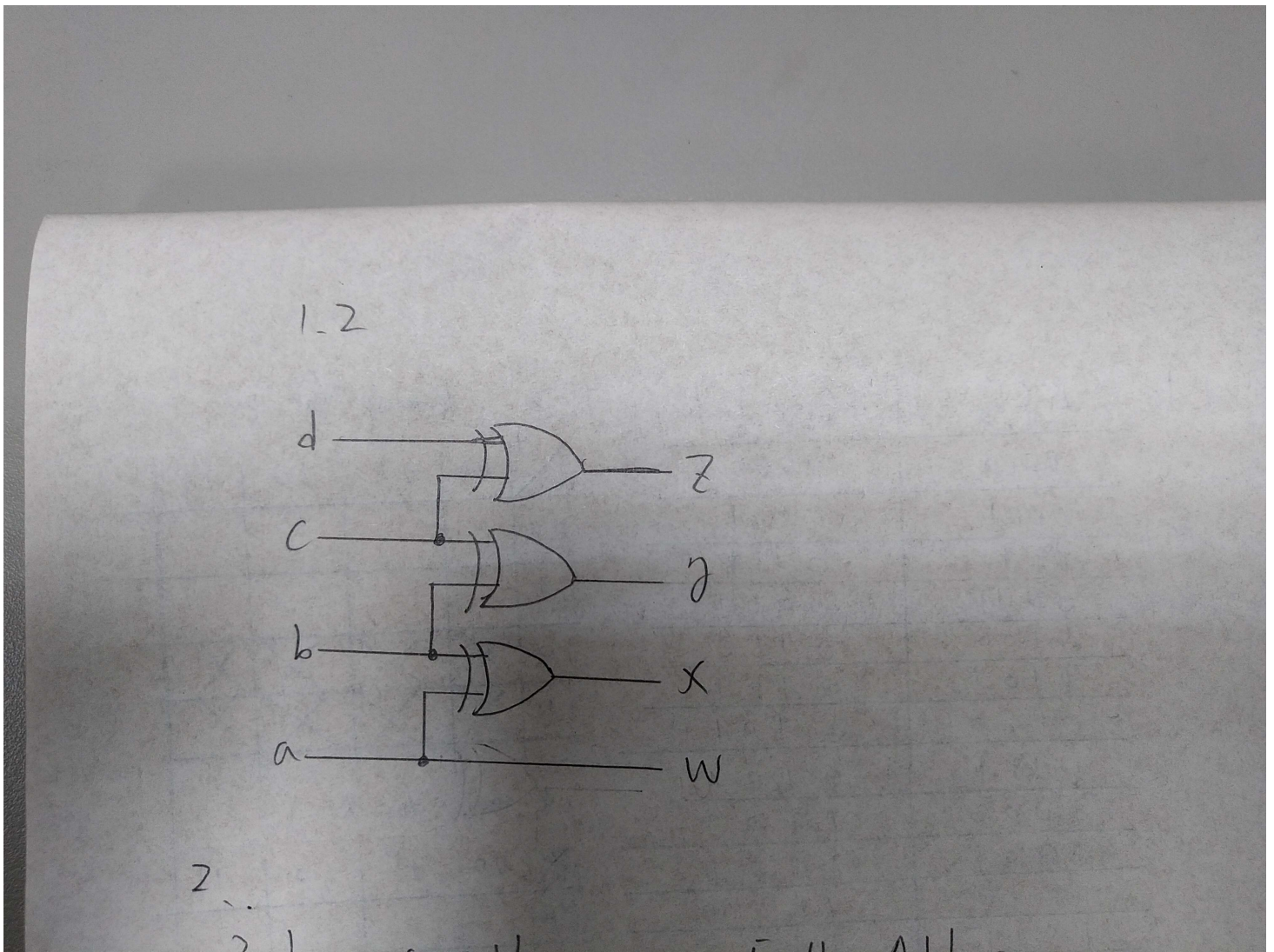

RTL Simulation

 

Lab 1 - 2: 4-Bit Adder-Subtractor

[Source Code](#)

Design Specification

Full Adder

Input: a, b, c_in

Output: sum, c_out

4-Bit Adder-Subtractor

Input [3:0]a, [3:0]b, m

Output [3:0]s, v

Design Implementation

Full Adder

For 1-bit addition, it would yield 0 when $1 + 1$ or $0 + 0$. Otherwise, it would yield 1. As a result, we can use XOR gate to implement the addition operation like the following code.

Boolean Equation:

$$\text{sum} = a \oplus b \oplus c_{\text{in}}$$

where c_{in} is the carry-in bit c_in.

Verilog Code

```
assign sum = (a ^ b) ^ c_in;
```

As for the carry bit, we've known that the carry bit would be 1 while two of the input bits: a, b and c_in (the carry bit of the previous one) are 1. Thus, we can express the Boolean equation as the follow

Boolean Equation:

$$c_{\text{out}} = (a \wedge b) \vee (c_{\text{in}} \wedge (a \oplus b))$$

where c_{in} is the carry-in bit c_in.

Verilog Code


```
assign c_out = (a & b) | c_in & (a ^ b);
```

Logic Diagram

2.

2.1 Half Adder


a	b	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$\text{Sum} = a \oplus b$$

$$\text{Carry} = a \cdot b$$

Full Adder

 

$$\text{Sum} = (a \oplus b) \oplus C_{in}$$

$$\text{Cout} = (a \cdot b) + ((a \oplus b) \cdot C_{in})$$

4-bit signed Adder

$$C_{in0} = m$$

$$S_0 = (a_0 \oplus (b_0 \oplus m)) \oplus C_{in0}$$

$$C_{out0} = (a_0 \cdot b_0) + ((a_0 \oplus b_0) \cdot C_{in0})$$

$$S_1 = (a_1 \oplus (b_1 \oplus m)) \oplus C_{out0}$$

$$C_{out1} = (a_1 \cdot b_1) + ((a_1 \oplus b_1) \cdot C_{out0})$$

$$S_2 = (a_2 \oplus (b_2 \oplus m)) \oplus C_{out1}$$

$$C_{out2} = (a_2 \cdot b_2) + ((a_2 \oplus b_2) \cdot C_{out1})$$

$$S_3 = (a_3 \oplus (b_3 \oplus m)) \oplus C_{out2}$$

$$C_{out3} = (a_3 \cdot b_3) + ((a_3 \oplus b_3) \cdot C_{out2})$$

$$V = (C_{out3} \oplus S_3) \cdot (\neg(a_3 \oplus b_3) \oplus m)$$

RTL Simulation



4-Bit Adder-Subtractor

As for 4-bit adder, all we need to do is that concatenate the 4 full-adder. Thanks to 2's complement. The full-adder also works when the input number is negative in the form of 2's complement. To adapt

the subtraction, we only need to invert the number and set the carry-in as 1.

```
wire C_IN;
wire C_OUT_0, C_OUT_1, c_OUT_2, c_OUT_3;
assign C_IN = m;
full_adder U0(.a(a[0]), .b(b[0] ^ m), .c_in(C_IN), .sum(s[0]), .c_out(C_OUT_0));
full_adder U1(.a(a[1]), .b(b[1] ^ m), .c_in(C_OUT_0), .sum(s[1]), .c_out(C_OUT_1));
full_adder U2(.a(a[2]), .b(b[2] ^ m), .c_in(C_OUT_1), .sum(s[2]), .c_out(C_OUT_2));
full_adder U3(.a(a[3]), .b(b[3] ^ m), .c_in(C_OUT_2), .sum(s[3]), .c_out(c_OUT_3));
```

However, we need to handle the overflow or underflow exceptions. We've known that the overflow might occur in 4 cases: (1) positive + positive, (2) negative + negative, (3) negative - positive, or (4) positive - negative. In this 4 cases, if we detect the last carry-out bit is different from the MSB of the summation, it means there is an overflow.

To detect the 4 possible cases:

$$\neg(a[3] \oplus b[3]) \oplus m$$

To detect the difference between carry out and the MSB.

$$c_{out} \oplus s[3]$$

where c_{out} is the last carry-out bit.

Boolean Equation:


$$v = (c_{out} \oplus s[3]) \wedge (\neg(a[3] \oplus b[3]) \oplus m)$$

Verilog Code

```
assign v = (c_OUT_3 ^ s[3]) & (~(a[3] ^ b[3]) ^ m);
```

Logic Diagram

2.2

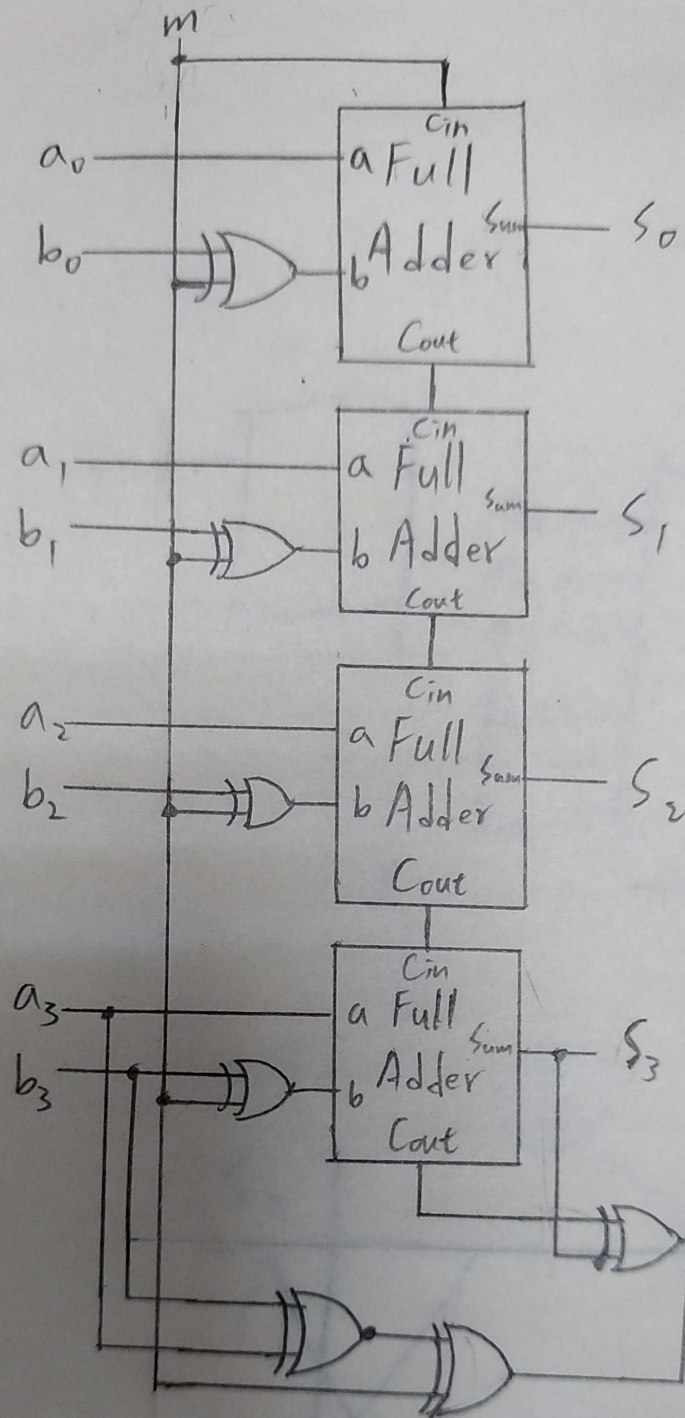

The logic diagram of the full adder is just like the circuit I've shown in the previous page.

3.

Multip

S	A	B
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$$Z = \sim S$$

A -

B -

S -

RTL Simulation



Lab 1 - 3: 3-Bit Signed Binary Max

Design Specification

[Source Code](#)

Full Adder

Input: a, b, c_in

Output: sum, c_out

3-Bit Adder-Subtractor

Input [2:0]a, [2:0]b, m

Output [2:0]s, v

Multiplexer

Input: a, b, s

Output: z

3-Bit Signed Binary Max

Input: [2:0]a, [2:0]b

Output: [2:0]o

Design Implementation

Full Adder

Same as the module in Lab 1-2.

3-Bit Adder-Subtractor

Same as the module in Lab 1-2.

Multiplexer(MUX)

In the file *mux.v*, it's just a 1-bit simple multiplexer. If *m* is 0, it would output the signal of input *a*, vice versa. Following are the Boolean equation and the code.

Boolean Equation

$$z = ((\neg s) \wedge a) \vee (a \wedge b) \vee (s \wedge (\neg a) \wedge b)$$

Verilog Code

```
assign z = ((~s) & a) | (a & b) | (s & (~a) & b);
```

Logic Diagram

3.

Multiplexer (Mux)


S \ AB	00	01	10	11
0			X	X
1		X		X

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$$Z = \sim S \cdot A + S \cdot A \cdot B + S \cdot \sim A \cdot B$$

Mux: 1 1 0 0 1

D-V
full
circuit
page.

 

RTL Simulation

 

3-Bit Signed Binary Max

It's easy to know that if the 2 number a and b have different sign, we only need to choose the positive one. Otherwise, we need to use the subtractor and let a minus b to determine which one is larger. If the MSB is 0, number a is larger. If the MSB is 1, number b is larger. We can simply form the Boolean equation of the multiplexer selection as the following.

Boolean Equation

$$SEL = (a[2] \wedge (\neg b[2])) \vee (a[2] \wedge S[2]) \vee ((\neg a[2]) \wedge (\neg b[2]) \wedge S[2])$$

where S is the difference between number a and b and SEL is the selection input of the multiplexer. To output the larger number, we only need to apply the multiplexer and the selection to each bit.

Verilog Code


```
wire [2:0]S;
wire M;
wire SEL;

assign M = 1;
bit3_add_sub U0(.a(a), .b(b), .m(M), .s(S));
assign minus = S;
assign SEL = (a[2] & (~b[2])) | (a[2] & S[2]) | ((~a[2]) & (~b[2]) & S[2]);


mux U1(.a(a[0]), .b(b[0]), .s(SEL), .z(o[0]));
mux U2(.a(a[1]), .b(b[1]), .s(SEL), .z(o[1]));
mux U3(.a(a[2]), .b(b[2]), .s(SEL), .z(o[2]));
```

Logic Diagram

I've shown in the previous page.

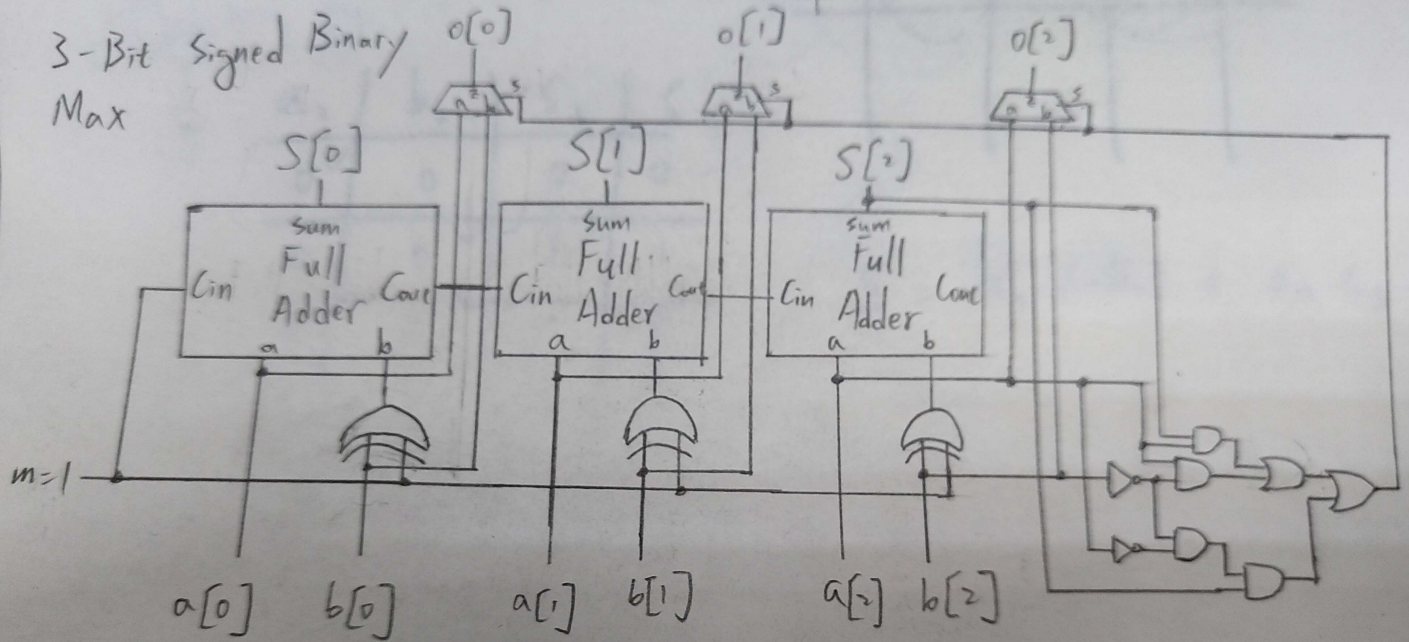

RTL Simulation

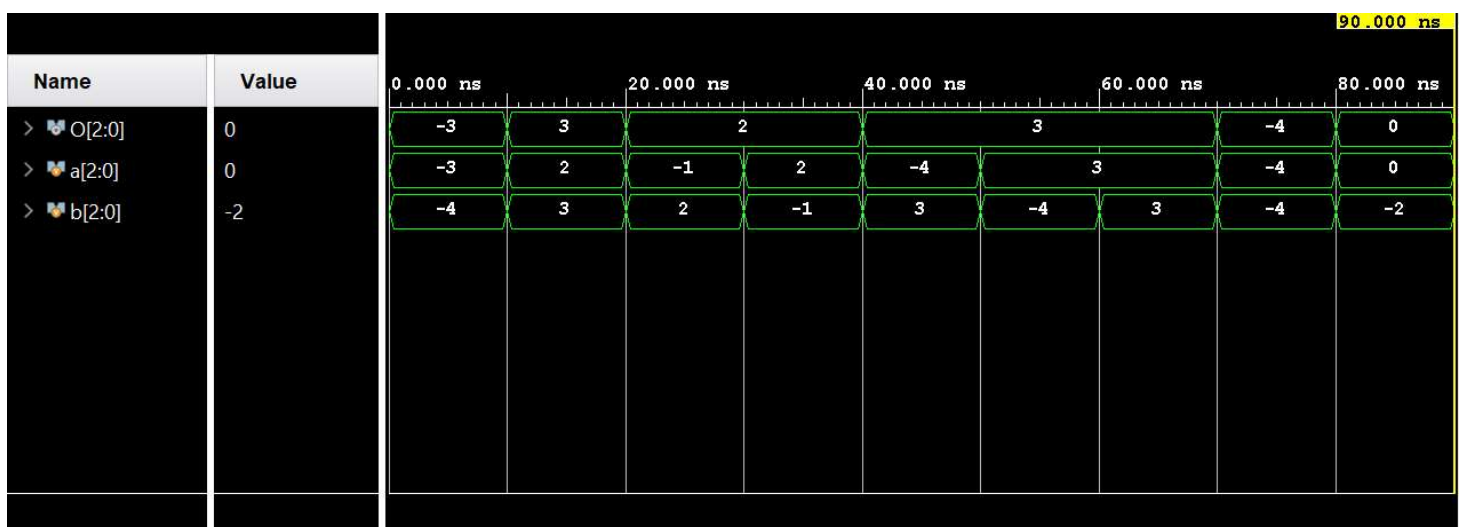

Discussion

In the lab 1-3, I used the star symbol * to express the AND logic and plus symbol + to represent the OR logic. However, the logical operator is totally different from the computational operator and the simulation shown that it was wrong. Finally, I found the misuse and correct the errors.

Conclusion

In this lab, I've learned that how to design a logical circuit with Verilog and simulate the behavior with RTL simulation. In addition, thanks for this lab, I reviewed the logic design briefly to recap the design of the full adder and Gray code.

Reference

- [Java T Point - Binary to Gray code conversion](#)

Provide the design example of the binary-to-Gray-code convertor.

- [GEEKSFORGEEKS - 4-bit binary Adder-Subtractor](#)

Provide the design example of the 4-bit binary Adder-Subtractor.

- [Electronics Tutorials - Binary Adder](#)

Provide the design example of the full adder.

- [Wikipedia - Two's complement](#)

Explain how the two's complement works.