

Lab 6 - Electronic Clock

106033233 資工大四 周聖諺 (Sheng-Yen Chou)

2022-04-15

Contents


Lab 6 - Electronic Clock Report	4
Block Diagram	4
Finite State Machine	4
Design Specification	4
Design Implementation	4
Time Display Module	5
Design Specification	5
Design Implementation	5
Unit Setting Module	6
Design Specification	6
Design Implementation	6
Alarm Module	6
Design Specification	6
Design Implementation	6
Stopwatch Module	7
Design Specification	7
Design Implementation	7
Switch Controller Module	7
Design Specification	7
Design Implementation	7
Display Controller Module	7
Design Specification	7
Design Implementation	8
Clock Generator Module	8
Design Specification	8
Design Implementation	8
Extract Module	8
Design Specification	8
Design Implementation	9
Scan Controller Module	9
Design Specification	9
Design Implementation	9
Display Module	9
Design Specification	9
Design Implementation	9

Debounce	10
Design Specification	10
Design Implementation	10
Onepule Module	10
Design Specification	10
Design Implementation	10
Counterx Module	10
Design Specification	10
Design Implementation	11
Datetime Limit Module	11
Design Specification	11
Design Implementation	11
Design Implementatio	11
I/O Pin Assignment	11
Conclusion	12

Lab 6 - Electronic Clock Report

106033233 資工大四 周聖謬 (Sheng-Yen Chou)

Block Diagram

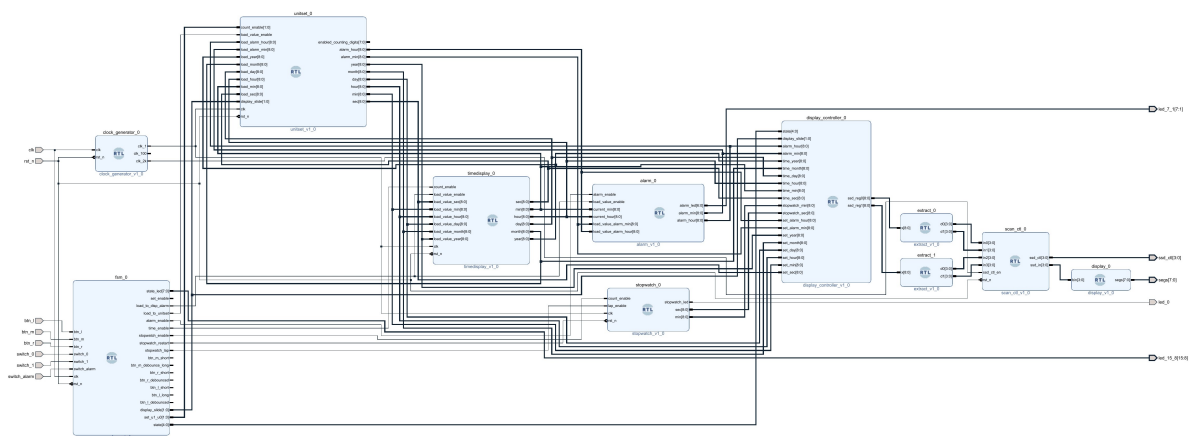

Finite State Machine

Design Specification

fsm.v Source Code

Output: [15:0] state_led, [1:0] display_slide, load_to_disp_alarm, load_to_unitset, time_enable, alarm_enable, stopwatch_enable, stopwatch_restart, stopwatch_lap, [1:0] set_u1_u0, [4:0] state

Input: btn_l, btn_m, btn_r, switch_0, switch_1, switch_alarm, clk, rst_n

Design Implementation

State Control

Use 3 DIP switches to control the states and the activation of the alarm and some variables only depend on the state, including `state`, `load_to_disp_alarm`, `load_to_unitset`, `time_enable`, and `alarm_enable`. The variable `load_to_disp_alarm` decides whether to load the output of the module `unitset` and `load_to_unitset` determine whether to load current digits of the alarm and the time components to module `unitset`. `load_to_disp_alarm` is on in the state `TIME` and `SET`.

Time Display and Alarm

The variables `time_enable` and `alarm_enable` control whether to enable counting of the modules. Absolutely, `time_enable` is enabled in state `TIME` and `alarm_enable` is enabled in state `ALARM`.

Stopwatch

The variables `stopwatch_enable`, `stopwatch_restart`, and `stopwatch_lap` control the behavior of the stopwatch module. The implementation is totally the same as the Lab 5-2. The finite state machine controls 2 signals: `stopwatch_enable` and `stopwatch_restart`. The down counter will pause while the signal `stopwatch_enable` is at low voltage and resume to count while the signal is at low voltage. It is controlled independently, so I only need to inverse the signal whenever the right button `btn_r` is pressed.

On the other hand, the down counter will reset to 0 when the signal `stopwatch_restart` raises. It only depends on `btn_l` button, so we only need to inverse the signal whenever the button is clicked.

Others

The variable `state_led` controls the LED display of the board and it can simply implemented by switch and if-else condition control.

`display_slide` controls the digits that would be displayed in the 7-segment display.

Time Display Module

Design Specification

timedisplay.v Source Code

Output: year, month, day, hour, min, sec

Input: `count_enable`, `load_value_enable`, `load_value_year`, `load_value_month`, `load_value_day`, `load_value_hour`, `load_value_min`, `load_value_sec`, `clk`, `rst_n`

Design Implementation

The module is implemented with a series of `counterx` module. We can simply cascade the `counterx` from the second to the year. Use the carry bit to trigger the next counter.

For leap year, I design a module called `datetime_limit` to count the length of a month. The module will set the length of February in the leap year as 29, otherwise, as 28.

Unit Setting Module

Design Specification

unitset.v Source Code

Output: [8:0] alarm_hour, [8:0] alarm_min, [8:0] year, [8:0] month, [8:0] day, [8:0] hour, [8:0] min, [8:0] sec

Input: count_enable, load_value_enable, [8:0] load_alarm_hour, [8:0] load_alarm_min, [8:0] load_year, [8:0] load_month, [8:0] load_day, [8:0] load_hour, [8:0] load_min, [8:0] load_sec, display_slide, clk, rst_n

Design Implementation

The `display_slide` will control the variable `enabled_counting_digits` to decide which unit to set up. While `display_slide` is 3, 2, 1, 0, the unitset will set the (alarm hour, alarm minute), (year, month), (day, hour) and, (minute, second) individually. The module also support leap years.

The module is implemented by a series of cascaded counters `counterx`. The counting of a digit would be enabled while the digit is selected by the `enabled_counting_digits`.

Alarm Module

Design Specification

alarm.v Source Code

Output: [6:0] alarm_led, [8:0] alarm_min, [8:0] alarm_hour

Input: alarm_enable, load_value_enable, [8:0] current_min, [8:0] current_hour, [8:0] load_value_alarm_min, [8:0] load_value_alarm_hour

Design Implementation

If `load_value_enable` is enabled, the module will load the argument `load_value_alarm_hour` to the register `alarm_hour` and load the argument `load_value_alarm_min` to the register `alarm_min`. In addition, while `alarm_enable` is enabled, the alarm will be active. If the current hour and minute is the same as the hours and the minute, `alarm_led` will be lighted up.

Stopwatch Module

Design Specification

stopwatch.v Source Code

Output: stopwatch_led, [8:0] sec, [8:0] min,

Input: count_enable, lap_enable, clk, rst_n

Design Implementation

The `stopwatch` module is implemented by 2 `counterx` modules. The counter will be activated while the argument `count_enable` is true. It will be reset while the argument `rst_n` is raised. In addition, while the argument `lap_enable` is true, the variable `sec` and `min` will be freezed and stopped to synchronize with the argument `counting_sec` and `counting_min`.

Switch Controller Module

Design Specification

switch_controller.v Source Code

Output: [8:0] sel_d1, [8:0] sel_d0

Input: [8:0] alarm_hour, [8:0] alarm_min, [8:0] year, [8:0] month, [8:0] day, [8:0] hour, [8:0] min, [8:0] sec, [1:0] display_slide

Design Implementation

The module will select the corresponding unit as output according to the `display_slide` argument. When `display_slide` is equal to 0, 1, 2, 3, the module will output (`sel_d1`, `sel_d0`) = (`alarm_hour`, `alarm_min`), (`year`, `month`), (`day`, `hour`), (`min`, `sec`) respectively.

Display Controller Module

Design Specification

display_controller.v Source Code

Output: [8:0] ssd_reg0, [8:0] ssd_reg1

Input: [4:0]state, [1:0]display_slide, [8:0] alarm_hour, [8:0] alarm_min, [8:0] time_year, [8:0] time_month, [8:0] time_day, [8:0] time_hour, [8:0] time_min, [8:0] time_sec, [8:0] stopwatch_min, [8:0] stopwatch_sec, [8:0] set_alarm_hour, [8:0] set_alarm_min, [8:0] set_year, [8:0] set_month, [8:0] set_day, [8:0] set_hour, [8:0] set_min, [8:0] set_sec

Design Implementation

The module will select corresponding inputs as the output according to the argument `state` and `display_slide`. First, the module will call `switch_controller` module to select the corresponding numbers according to the argument `display_slide`. Then, The module will choose the numbers that will be shown in the 7-segment display `ssd_reg0` and `ssd_reg1` from the selected numbers. While the `state[4:3]` is equal to 2'b00(Time), 2'b11(SET), and 2'b01(STW), the module will choose the selected number of `timedisplay`, `unitset`, and `stopwatch` respectively.

Clock Generator Module

Design Specification

clock_generator.v Source Code

Output: reg clk_1, reg clk_100, reg clk_2k,

Input: clk, rst_n

Design Implementation

The clock generator provides 1 Hz clock and 100 Hz clock. The module is implemented by a counter. Whenever the counter hit the limit, the module would invert the output signal.

Extract Module

Design Specification

extract.v Source Code

Output: [3:0] d0, [3:0] d1

Input: [8:0] x

Design Implementation

The `extract` module will separate the tens digit `d1` and unit digits `d0` from the input number `x`.

Scan Controller Module

Design Specification

scan_ctl.v Source Code

Output: [3:0] `ssd_in`, [3:0] `ssd_ctl`

Input: [3:0] `in0`, [3:0] `in1`, [3:0] `in2`, [3:0] `in3`, `ssd_ctl_en`, `rst_n`

Design Implementation

Since we can only control one digit of the 7-segment display each time, I design a module that takes the 4-digit patterns as input and shows the 1 digit on the display when the clock raises. Whenever the clock raises, the module will switch the control `ssd_ctl` to different digit and shows the corresponding digit. Take an example, when the first clock raise occur, the module will set `ssd_ctl` = 4' `b1110` and `ssd_in` = `in0`. As for second clock pulse, the module will output `ssd_ctl` = 4' `b1101` and `ssd_in` = `in1` and so on.

Display Module

Design Specification

display.v Source Code

Output: [7:0] `segs`

Input: [3:0] `bin`

Design Implementation

The module will convert the 4-bits binary number to 7-segment display patters from 0~16.

Debounce

Design Specification

debounce.v Source Code

Output: push_debounced

Input: rst, clk, push

Design Implementation

For each click, the module will delay 4 clock cycle and then raise the debounce pulse. I use 4 registers to represent the delay state and send a pulse while 4 registers are all 1s

Onepulse Module

Design Specification

onepulse.v Source Code

Output: push_onepulse, push_onepulse_long, push_debounced, push_debounced_long

Input: clk, rst, push

Design Implementation

The one-pulse module raise a pulse while the debounce module raises a pulse. As a result, it will produce high voltage while the previous debounce signal is higher than the current debounce signal.

Counterx Module

Design Specification

counterx.v Source Code

Output: [8:0] q, time_carry, count_enable, load_value_enable, [8:0] load_value, [8:0] count_limit_u, [8:0] count_limit_l, [8:0] count_init

Input: clk, rst_n

Design Implementation

The `counterx` module is a binary-up counter that counts from `count_limit_l` to `count_limit_u`. The argument `count_init` set the initial value of the counter.

Datetime Limit Module

Design Specification

datetime_limit.v Source Code

Output: [8:0] year_limit, [8:0] month_limit, [8:0] day_limit, [8:0] hour_limit, [8:0] min_limit, [8:0] sec_limit, [8:0] year_init, [8:0] month_init, [8:0] day_init, [8:0] hour_init, [8:0] min_init, [8:0] sec_init

Input: [8:0] year, [8:0] month

Design Implementation

The module provide the upper limit of each date/time unit and support leap year. During the leap year, the length of February is 29, otherwise is 28.

Design Implementatio

I/O Pin Assignment

I/O	switch_0	switch_0	switch_alarm	btn_m
LOC	V17	V16	R2	T18

I/O	clk	rst	btn_r	btn_l	ssd_ctl[0]	ssd_ctl[1]	ssd_ctl[2]	ssd_ctl[3]
LOC	W5	W16	T17	W19	U2	U4	V4	W4

I/O	segs[0]	segs[1]	segs[2]	segs[3]	segs[4]	segs[5]	segs[6]	segs[7]
LOC	V7	U7	V5	U5	V8	U8	W6	W7

I/O	led[0]	led[1]	led[2]	led[3]	led[4]	led[5]	led[6]	led[7]
LOC	U16	E19	U19	V19	W18	U15	U14	V14

I/O	led[8]	led[9]	led[10]	led[11]	led[12]	led[13]	leds[14]	led[15]
LOC	V13	V3	W3	U3	P3	N3	P1	L1

Conclusion

In lab6, I firstly implement a large project, which is more than 1000 lines of codes. I spent lots of time on the `unitset` module and how to design a data flow between the `timedisplay`, `alarm`, and `unitset`. I've learned a lot while doing this homework.